

Jiangxi University of Science and Technology

# DIGITAL DESIGN

## Lecture 11: The Karnaugh Map\_2 Minimization





# Small Review: Karnaugh Maps (K-Maps)

- A visual way to simplify logic expressions
- It gives the most simplified form of the expression
- Simplification of logic expression using Boolean algebra is awkward because:
  - it lacks specific rules to predict the most suitable next step in the simplification process
  - it is difficult to determine whether the simplest form has been achieved.



# Don't-Care Conditions

- Some logic circuits can be designed so that there are certain input conditions for which there are no specified output levels.
- A circuit designer is free to make the output for any don't care condition either a 0 or a 1 in order to produce the simplest output expression.




# Don't Care Conditions

- In some circuits we care only about the output for some combinations of input values, because other combinations of input values are not possible or never occur. This gives us freedom in producing a simple circuit with the desired output because the output values for all those combinations that never occur can be arbitrarily chosen.
- The values of the function for these combinations are called don't care conditions. A  $d$  is used in a K-map to mark those combinations of values of the variables for which the function can be arbitrarily assigned.
- In the minimization process we can assign 1s as values to those combinations of the input values that lead to the largest blocks in the K-map.

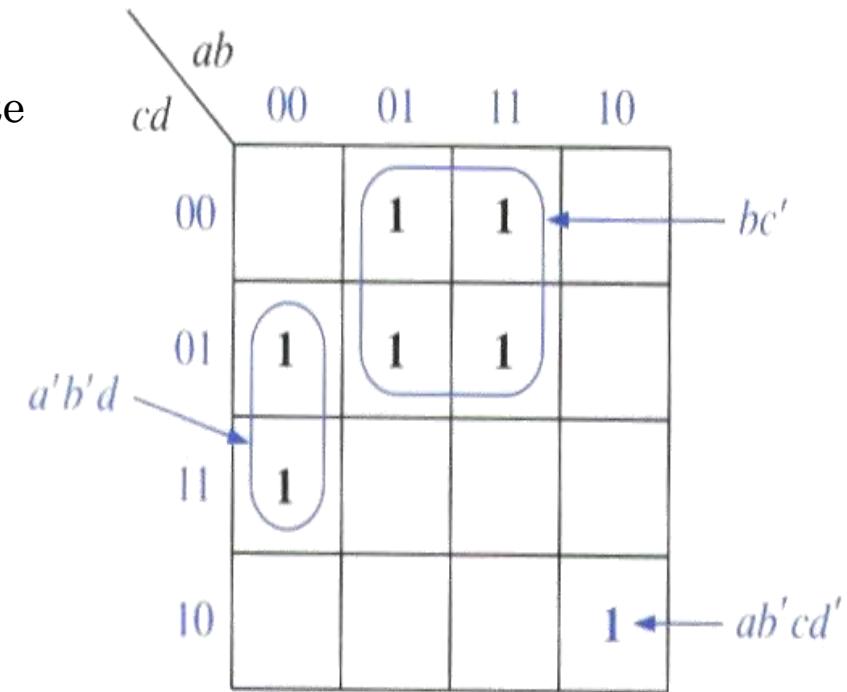
# Simplification Example

Minterms are combined in groups of 2, 4, or 8 to eliminate 1, 2, 3 variables.  
Corner terms.



$$\begin{aligned}f_1 &= \Sigma m(1, 3, 4, 5, 10, 12, 13) \\&= bc' + a'b'd + ab'cd'\end{aligned}$$

(a)

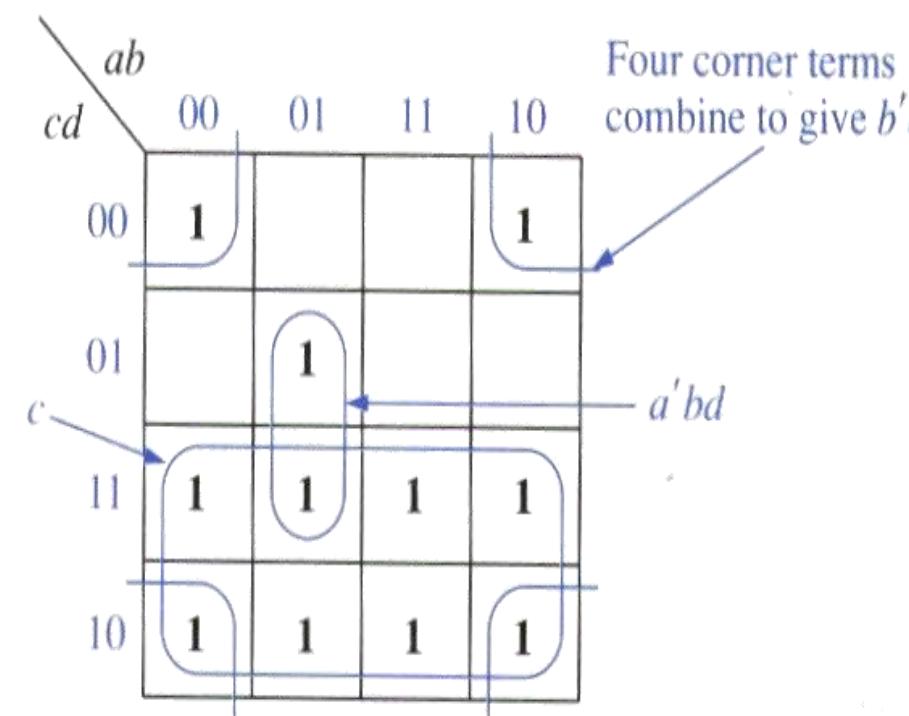


$$\begin{aligned}f_2 &= \Sigma m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15) \\&= c + b'd' + a'bd\end{aligned}$$

(b)
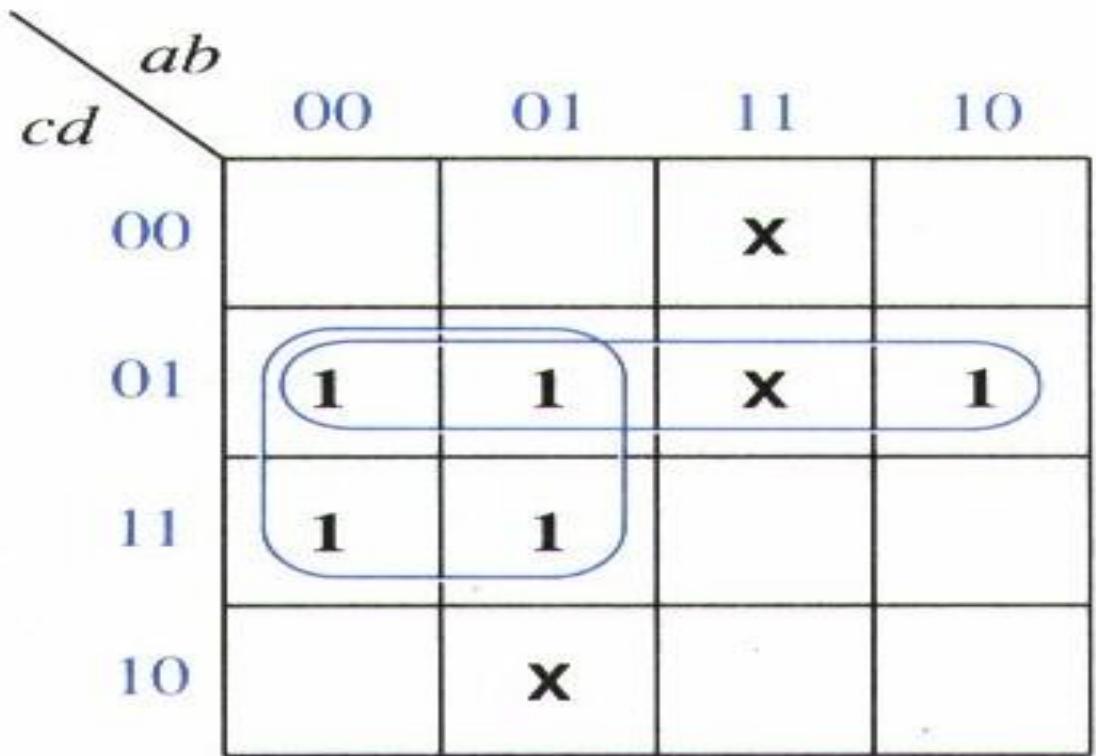
# Simplification with Don't Care

- Don't care “x” is covered if it helps.  
Otherwise leave it along.

$$f = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$$



$$\begin{aligned}
 f &= \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13) \\
 &= a'd + c'd
 \end{aligned}$$




# Determination of Minimum Expressions Using Essential Prime Implicants


- Definitions:
  - **Implicants:** An implicant of a function F is a single element of the on set (1) or any group of elements that can be combined together in a K-map.
  - **Prime Implicants:** An implicant that cannot be combined with another to eliminate a literal.
  - **Essential Prime Implicants:** If a particular element of the on-set is covered by a single prime implicant. That implicant is called an essential prime implicant.
- All essential primes must be part of the minimized expression.
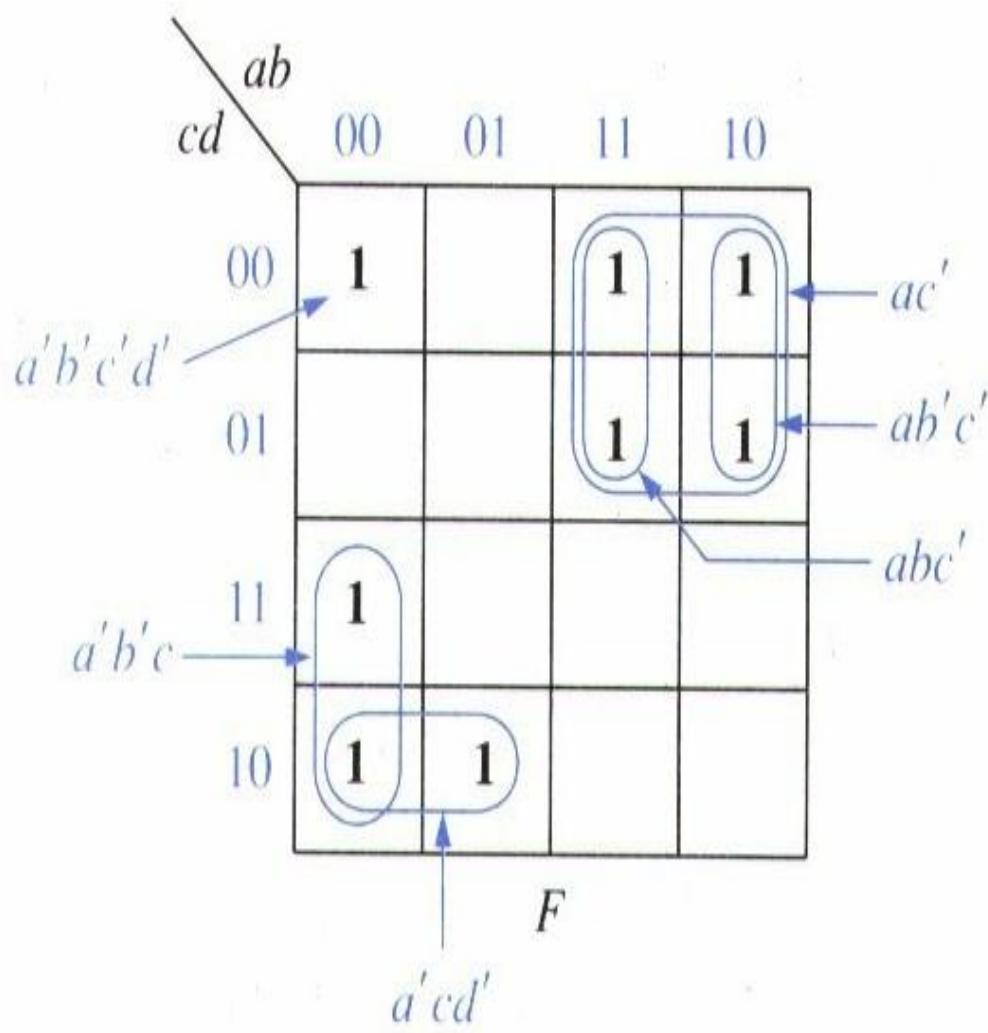
# Implicant of F

- Implicant
  - Any single 1 or any group of 1's
- Prime implicant
  - An implicant that can not be combined with another term to eliminate a variable.
    - $a'b'c$ ,  $a'cd'$ ,  $ac'$  are prime implicant.
    - $a'b'c'd'$  is not (combined with  $a'b'cd'$ ).  $abc'$  and  $ab'c'$  are not.



# Prime Implicant

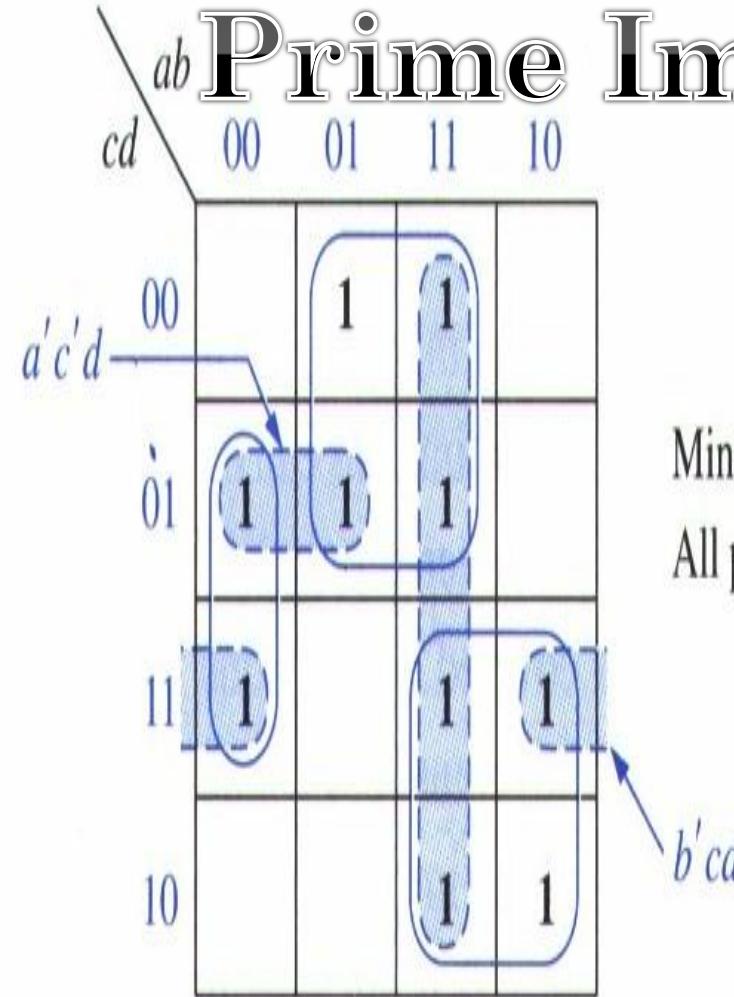


Minimum solution:  $F = a'b'd + bc' + ac$


All prime implicants:  $a'b'd, bc', ac, a'c'd, ab, b'cd$

- A single 1 which is not adjacent to any other 1's.
- Two adjacent 1's which are not contained in a group of four 1's. And so on.
  - Shaded loops are also prime implicants, but not part of the minimum solution.
  - $a'c'd$  and  $b'cd$  are already covered by other group. So we do not need them.
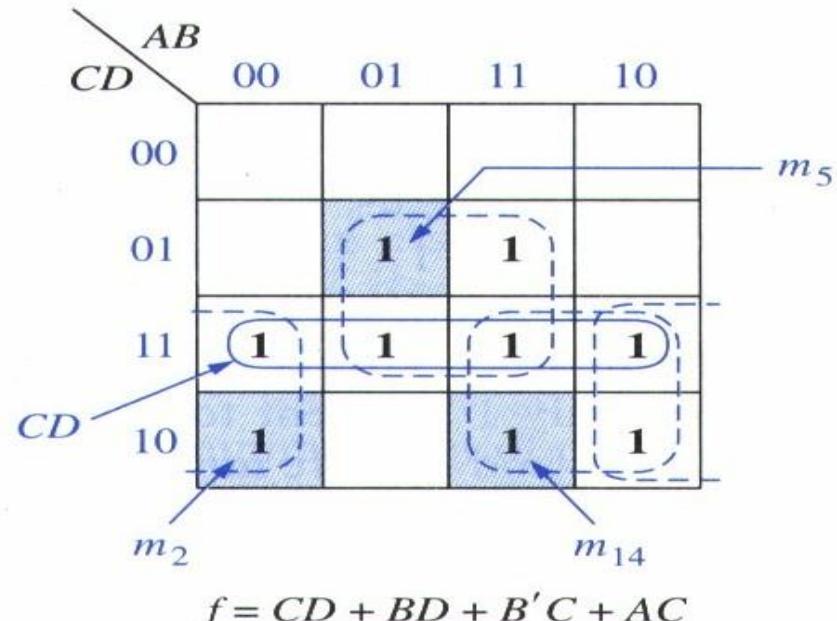
# Essential Prime Implicants for Minimum SOP



(a)

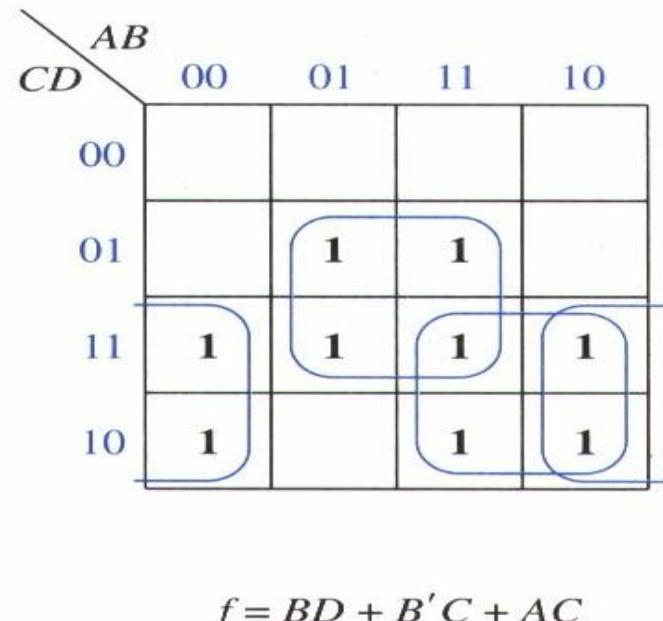


(b)

- If CD is chosen first, then f has 4 terms. We don't need CD since it is covered by other group. CD is not a essential prime implicant.
- m<sub>2</sub> is essential prime implicant since it is covered only by one prime implicant. So does m<sub>5</sub>, and m<sub>14</sub>. We need them in the answer.
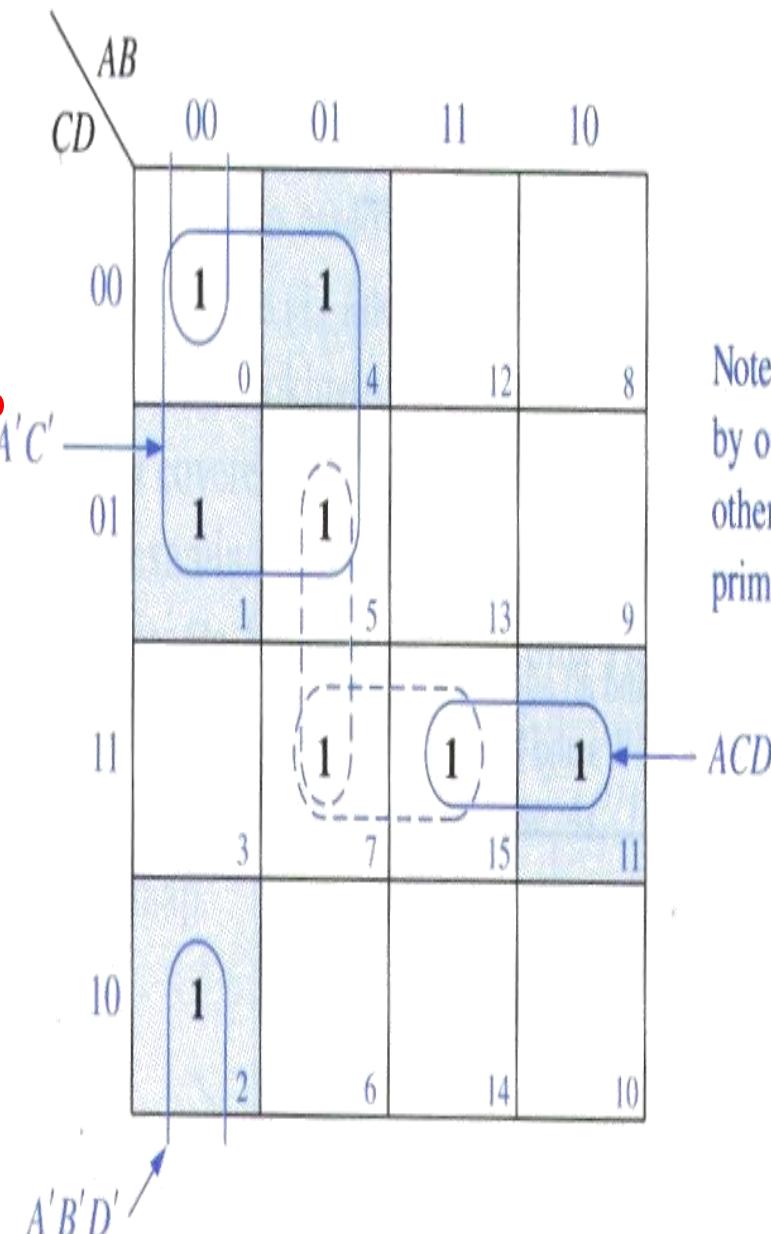
# Rule of Thumb

- Look at all squares adjacent to a minterm.

- If the given minterm and all of the 1's adjacent to it are covered by a single term, then that term is an essential prime implicant
- But if it is covered by more than two prime implicant, we can not tell whether this term is essential or not.
- The solution is  $A'C' + A'B'D' + ACD + (A'BD \text{ or } BCD)$ .



Note: 1's shaded in blue are covered by only one prime implicant. All other 1's are covered by at least two prime implicants.

# Four-Variable K-Maps

	CD	00	01	11	10
AB	00	1	0	0	0
00	00	0	0	0	0
01	01	0	1	0	0
11	11	0	1	0	0
10	10	0	0	0	0

$$f = \sum(0,8) = \bar{B} \bullet \bar{C} \bullet \bar{D}$$

	CD	00	01	11	10
AB	00	0	0	0	0
00	00	0	1	0	0
01	01	0	0	0	0
11	11	0	1	0	0
10	10	0	0	0	0

$$f = \sum(5,13) = B \bullet \bar{C} \bullet D$$

	CD	00	01	11	10
AB	00	0	0	0	0
00	00	0	0	0	0
01	01	0	0	0	0
11	11	0	1	1	0
10	10	0	0	0	0

$$f = \sum(13,15) = A \bullet B \bullet D$$

	CD	00	01	11	10
AB	00	0	0	0	0
00	00	0	0	0	0
01	01	1	0	0	1
11	11	0	0	0	0
10	10	0	0	0	0

$$f = \sum(4,6) = \bar{A} \bullet B \bullet \bar{D}$$

	CD	00	01	11	10
AB	00	0	0	1	1
00	00	0	0	1	1
01	01	0	0	0	0
11	11	0	0	0	0
10	10	0	0	0	0

$$f = \sum(2,3,6,7) = \bar{A} \bullet C$$

	CD	00	01	11	10
AB	00	0	0	0	0
00	00	1	0	0	1
01	01	0	0	0	1
11	11	1	0	0	1
10	10	0	0	0	0

$$f = \sum(4,6,12,14) = B \bullet \bar{D}$$

	CD	00	01	11	10
AB	00	0	0	1	1
00	00	0	0	0	0
01	01	0	0	0	0
11	11	0	0	0	0
10	10	0	0	1	1

$$f = \sum(2,3,10,11) = \bar{B} \bullet C$$

	CD	00	01	11	10
AB	00	1	0	0	1
00	00	1	0	0	0
01	01	0	0	0	0
11	11	0	0	0	0
10	10	1	0	0	1

$$f = \sum(0,2,8,10) = \bar{B} \bullet \bar{D}$$



# Four-Variable K-Maps



	CD	00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$f = \sum(4, 5, 6, 7) = \overline{A} \bullet B$$

	CD	00	01	11	10
AB	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	0

$$f = \sum(3, 7, 11, 15) = C \bullet D$$

	CD	00	01	11	10
AB	00	1	0	1	0
	01	0	1	0	1
	11	1	0	1	0
	10	0	1	0	1

$$f = \sum(0, 3, 5, 6, 9, 10, 12, 15)$$

$$f = A \otimes B \otimes C \otimes D$$

	CD	00	01	11	10
AB	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

$$f = \sum(1, 2, 4, 7, 8, 11, 13, 14)$$

$$f = A \oplus B \oplus C \oplus D$$

	CD	00	01	11	10
AB	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$f = \sum(1, 3, 5, 7, 9, 11, 13, 15)$$

$$f = D$$

	CD	00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1

$$f = \sum(0, 2, 4, 6, 8, 10, 12, 14)$$

$$f = \overline{D}$$

	CD	00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$f = \sum(4, 5, 6, 7, 12, 13, 14, 15)$$

$$f = B$$

	CD	00	01	11	10
AB	00	1	1	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1


$$f = \sum(0, 1, 2, 3, 8, 9, 10, 11)$$

$$f = \overline{B}$$



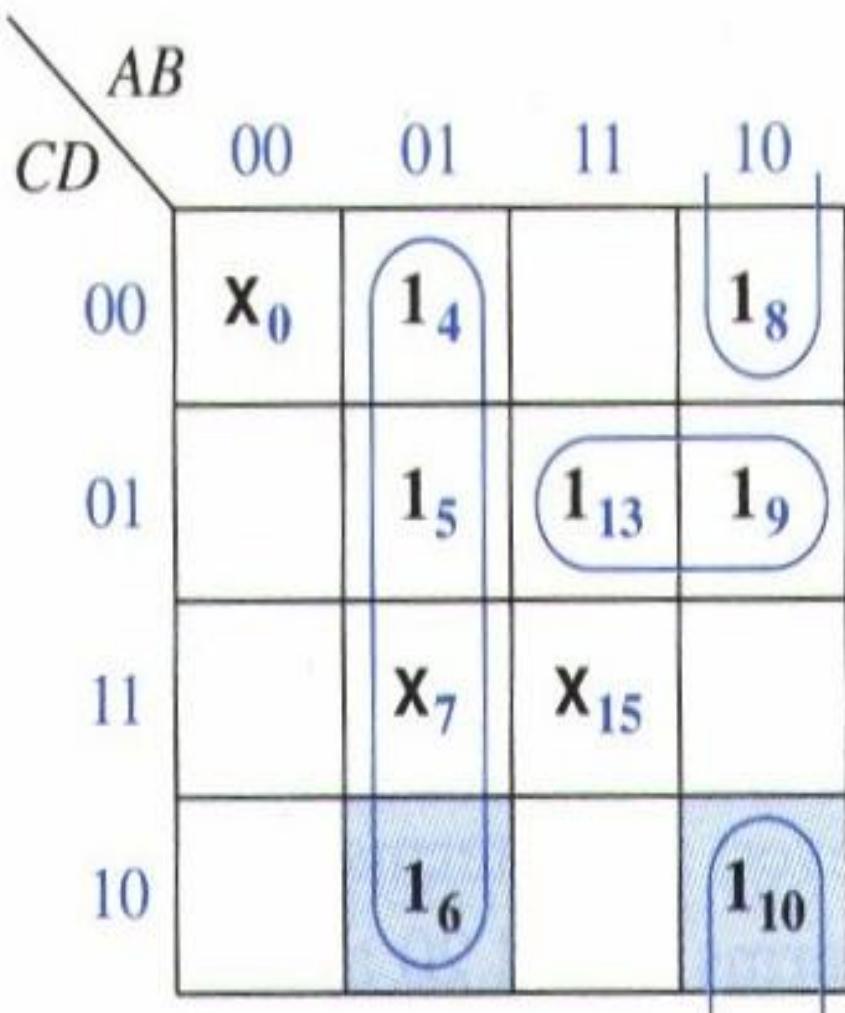
# Example

- Find the 1 that is covered by only one term first  
(Do not share with other circle).



Shaded 1's are covered by only one prime implicant


# 5-Variable K Map

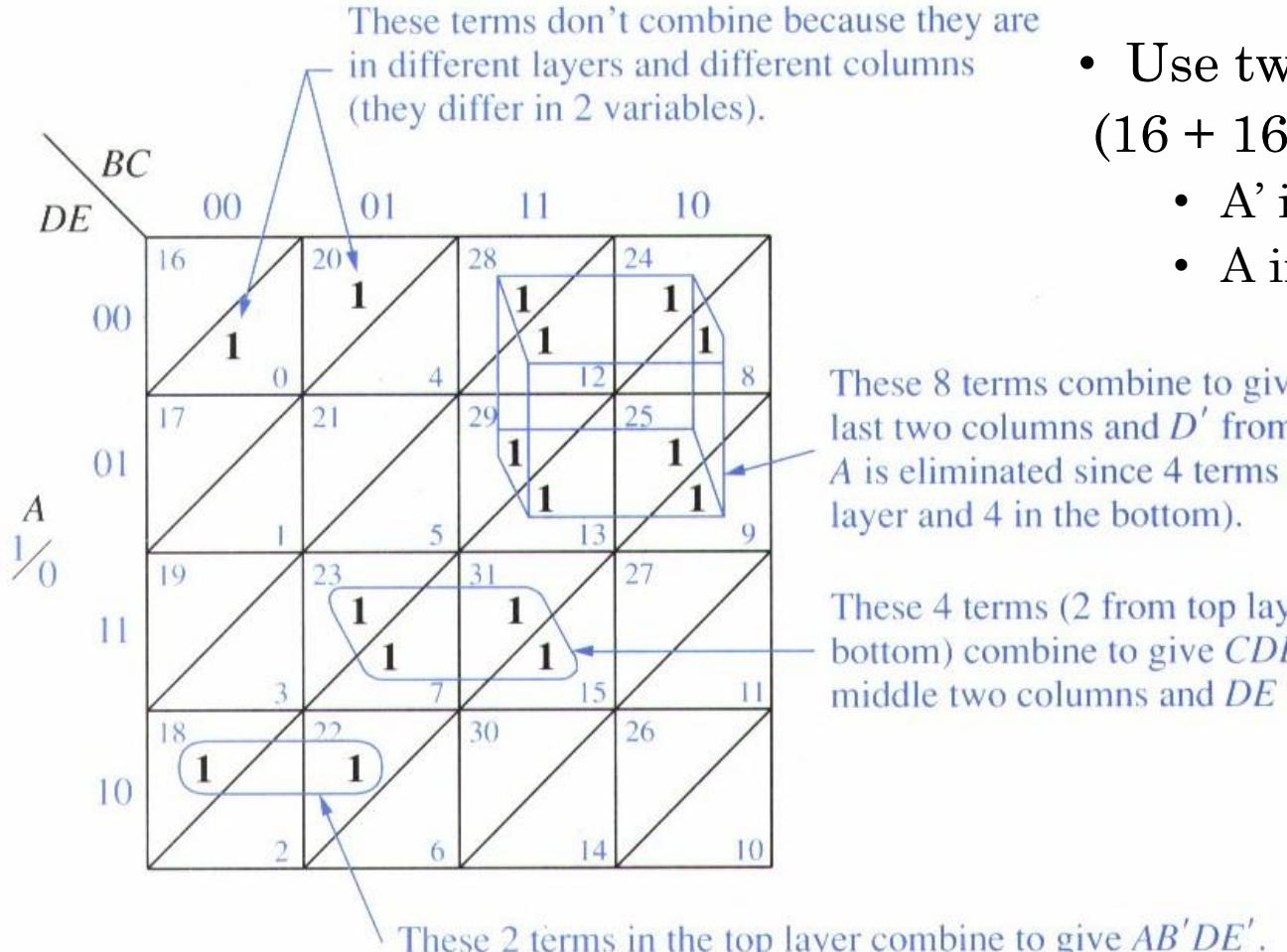


- Use two 4-variable map to form a 5-variable K map ( $16 + 16 = 32$ ) (A,B,C,D,E)
  - $A'$  in the bottom layer
  - $A$  in the top layer.

# 5 Neighbors

- Same plane and above or under

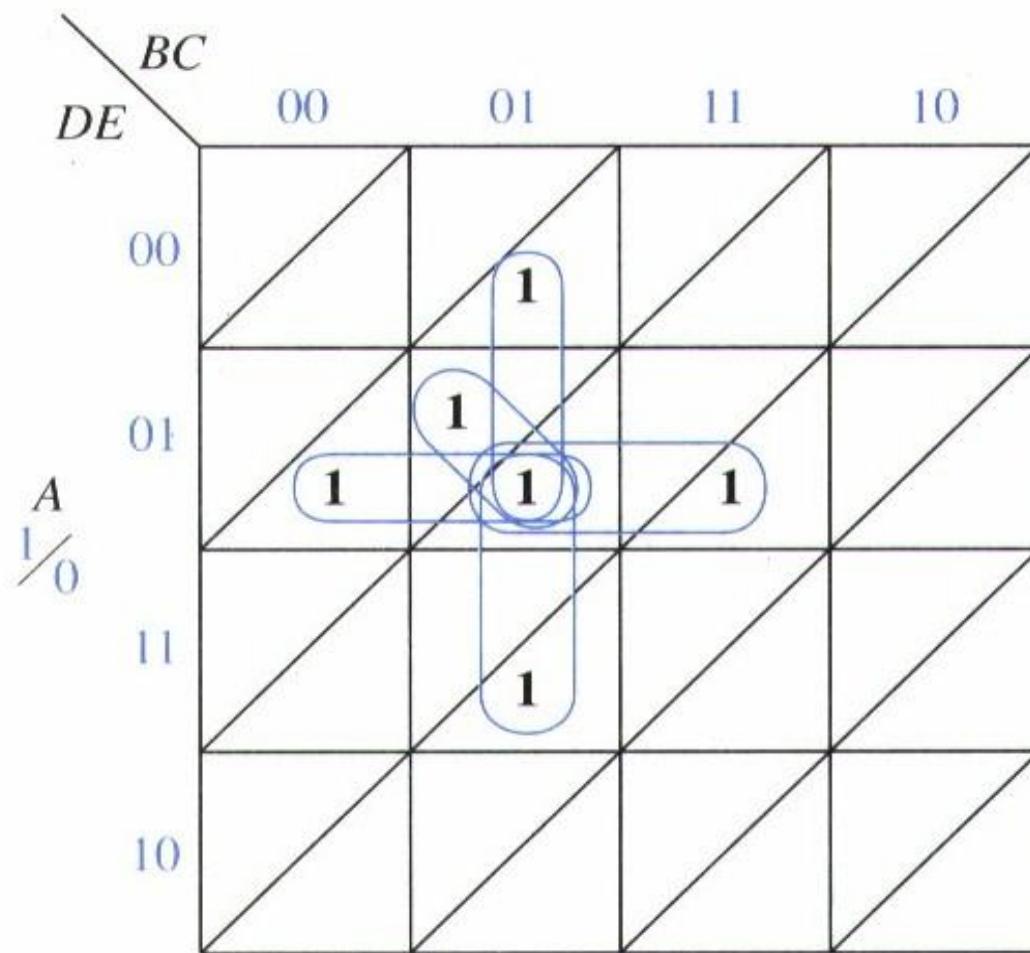

# Example: 5-variables

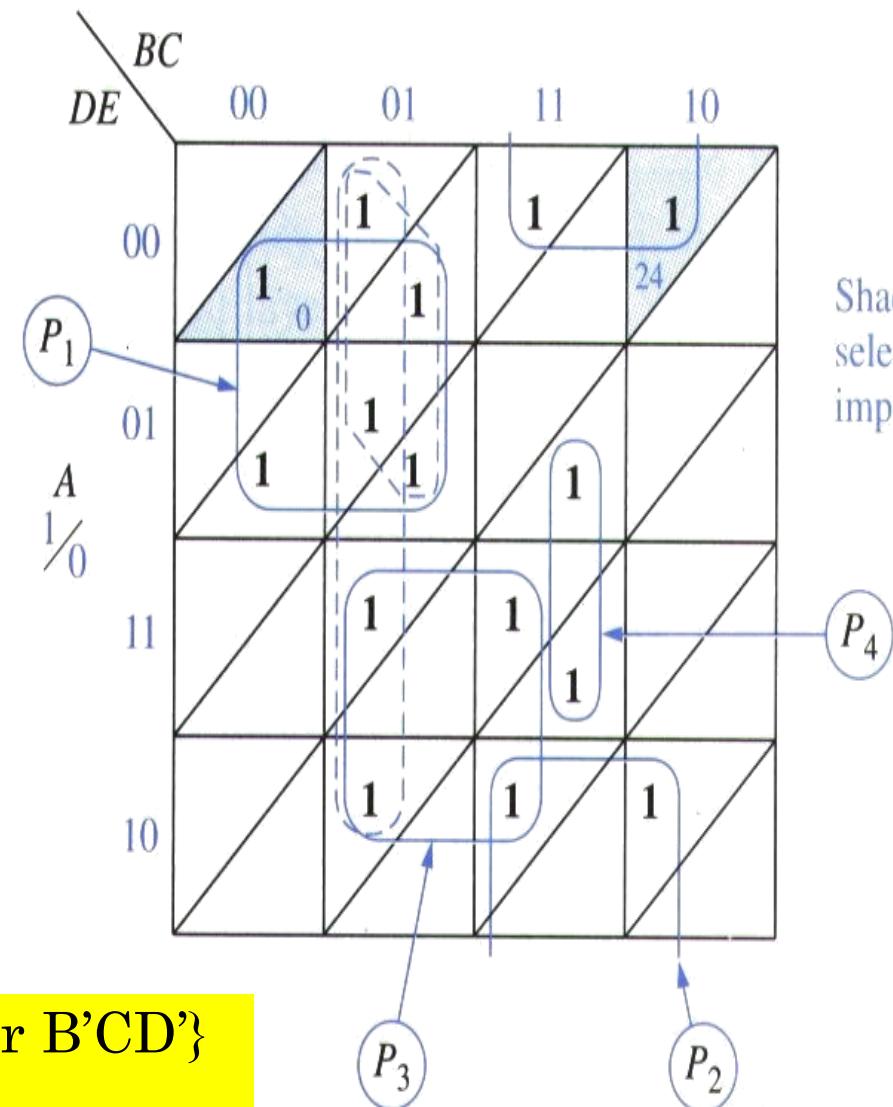


Shaded 1's are used to select essential prime implicants.

- Ans:  $F = A'B'D' + ABE' + ACD + A'BCE + \{AB'C \text{ or } B'CD'\}$ 
  - $P_1 + P_2 + P_3 + P_4 + AB'C \text{ or } B'CD'$
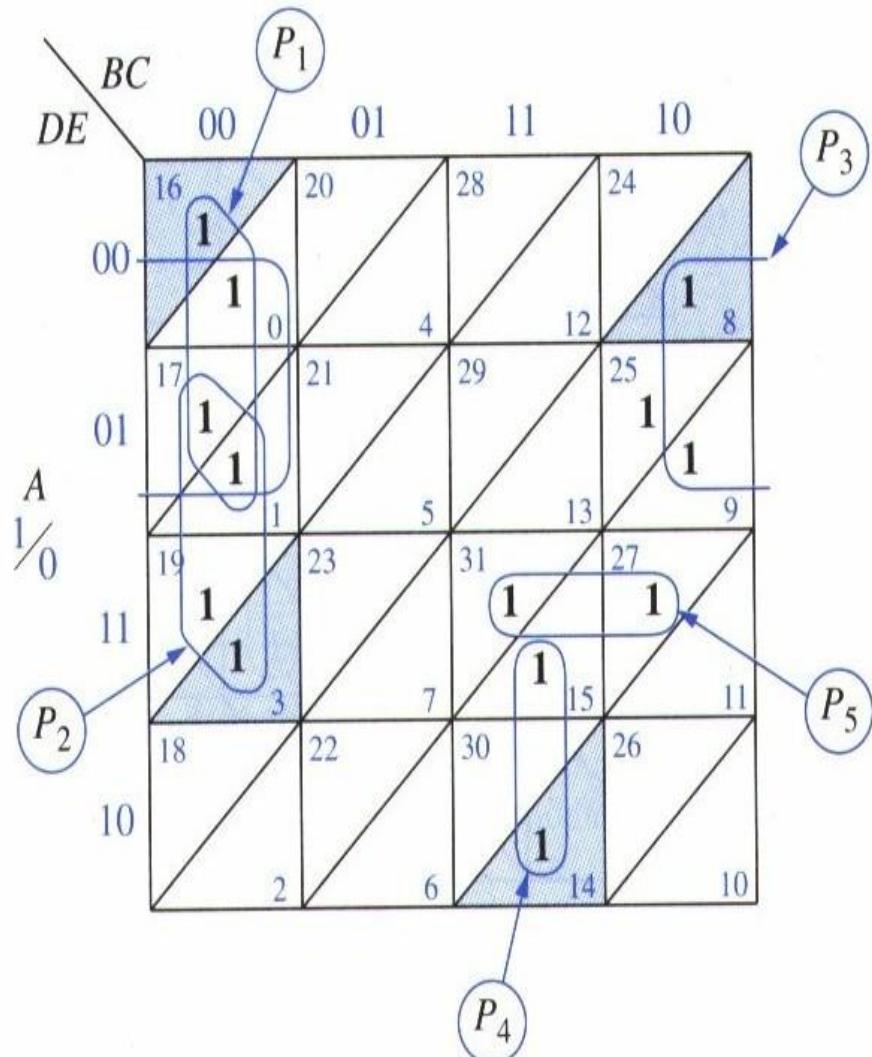
# One More

$$F = B'C'D' + B'C'E + A'C'D' + A'BCD + ABDE + \{C'D'E \text{ or } AC'E\}$$

$(17,19,25,27 = AC'E), (1,9,17,25 = C'D'E)$



# Simplification Using Map-Entered Variables

- Extend K-map for more variables.

- When E appears in a square, if  $E = 1$ , then the corresponding minterm is present in the function G.
- $G(A,B,C,D,E,F) = m_0 + m_2 + m_3 + Em_5 + Em_7 + Fm_9 + m_{11} + m_{15} + (\text{don't care terms})$

		AB	00	01	11	10
		CD	00			
00	01	1				
		X	E	X	F	
11	10	1	E	1	1	
		1				X

*G*

		AB	00	01	11	10
		CD	00			
00	01	1				
		X			X	
11	10	1			1	1
		1				X

$E = F = 0$

$$MS_0 = A'B' + ACD$$

		AB	00	01	11	10
		CD	00			
00	01	X				
		X	1		X	
11	10	X	1	X	X	
		X				X

$E = 1, F = 0$

$$MS_1 = A'D$$

		AB	00	01	11	10
		CD	00			
00	01	X				
		X		X	1	
11	10	X		X	X	
		X				X

$E = 0, F = 1$

$$MS_2 = AD$$

(a)


(b)

(c)

(d)
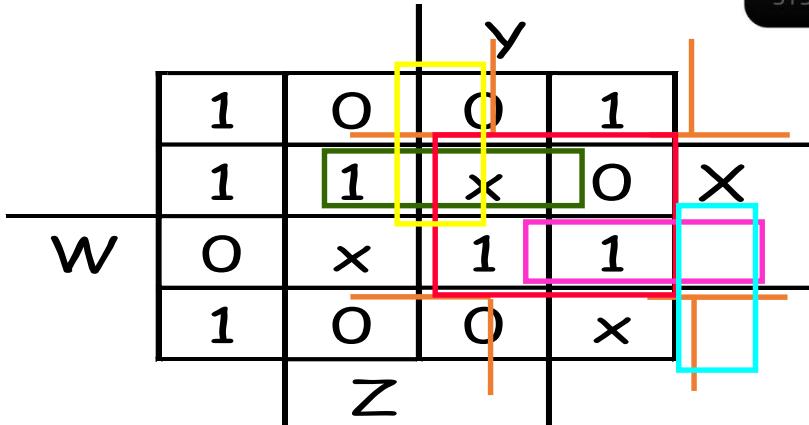
# Solutions for practice K-map 3

- Find a MSP for:  $f(w,x,y,z) = \Sigma m(0,2,4,5,8,14,15)$ ,  $d(w,x,y,z) = \Sigma m(7,10,13)$




All prime implicants are circled. We can treat X's as 1s if we want, so the red group includes two X's, and the light blue group includes one X.

The *only* essential prime implicant is  $x'z'$ . The red group is not essential because the minterms in it also appear in other groups.


The MSP is  $x'z' + wxy + w'xy'$ . It turns out the red group is redundant; we can cover all of the minterms in the map without it.
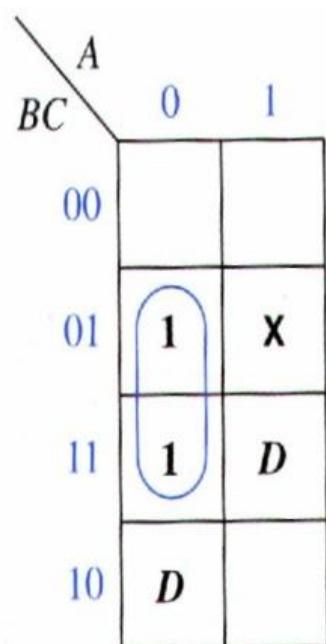
# Map-Entered Variable


- $F(A,B,C,D) = A'B'C + A'BC + A'BC'D + ABCD + (AB'C)$ , (don't care)
  - Choose D as a map-entered variable.
  - When  $D = 0$ ,  $F = A'C$  (Fig. a)
  - When  $D = 1$ ,  $F = C + A'B$  (Fig. b)
    - two 1's are changed to x's since they are covered in Fig. a.
- $F = A'C + D(C+A'B) = A'C + CD + A'BD$



(a)

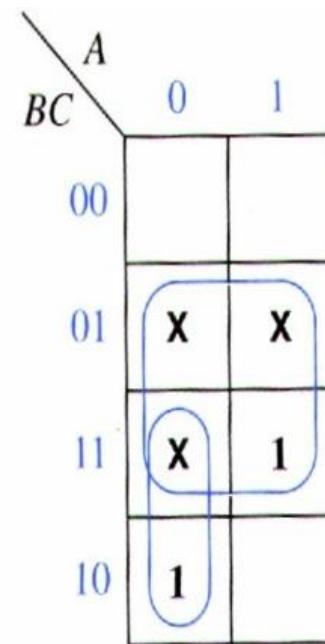

(b)

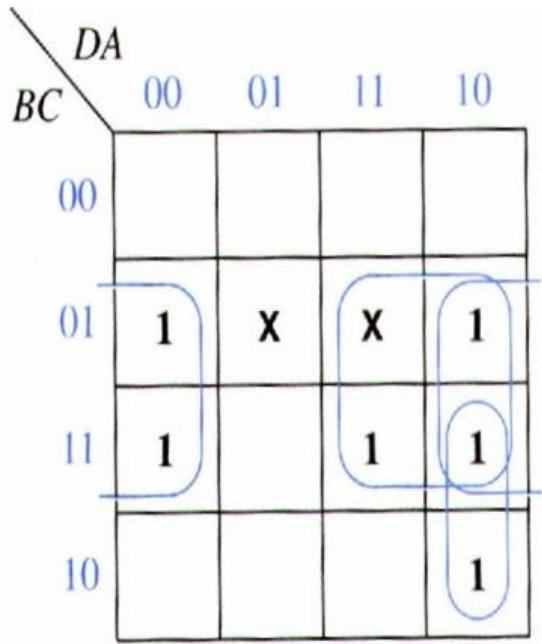

(c)



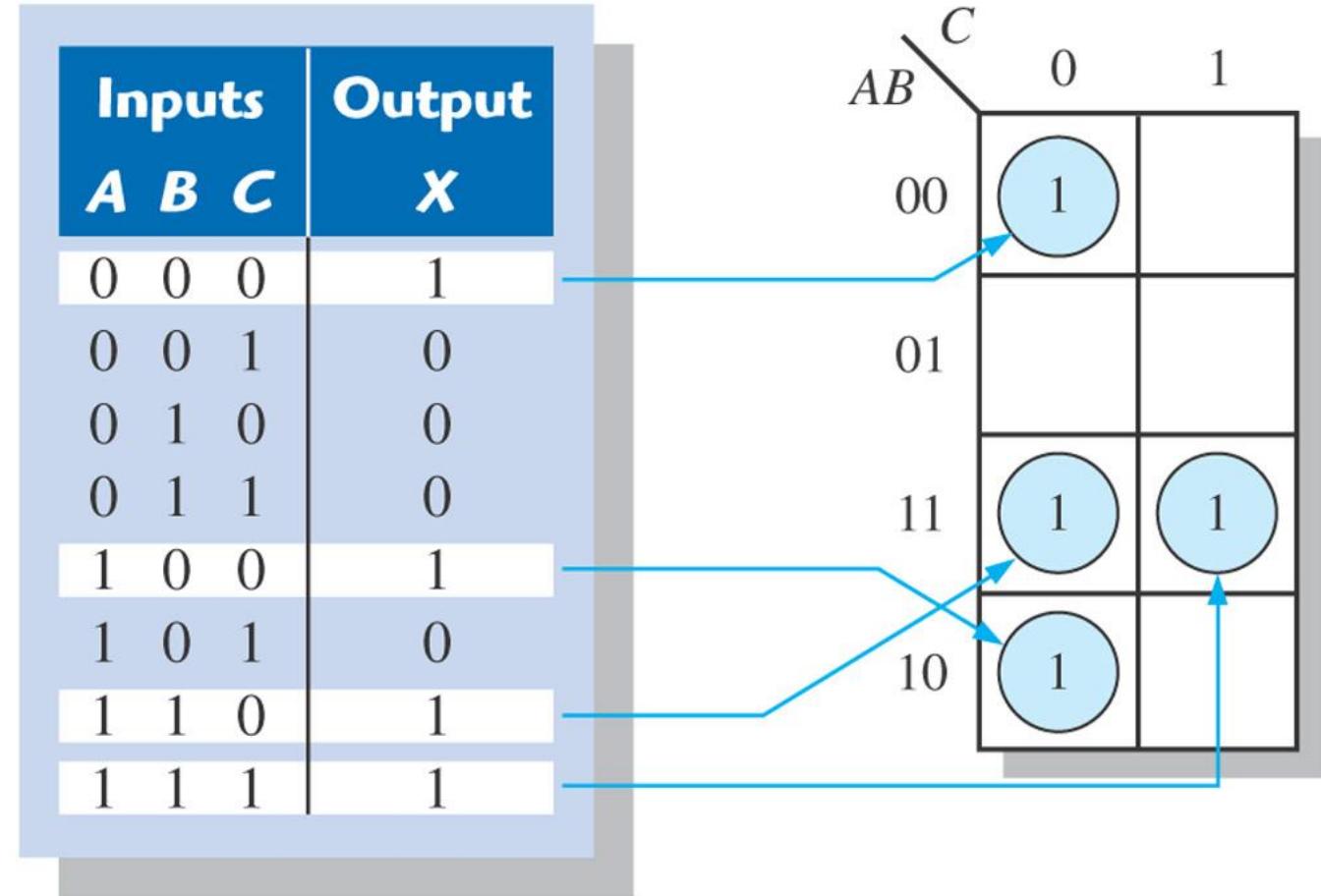
# General View for Map-Entered Variable Method

- Given a map with variables P<sub>1</sub>, P<sub>2</sub> etc, entered into some of the squares, the minimum SOP form of F is as follows:
- F = MS<sub>0</sub> + P<sub>1</sub> MS<sub>1</sub> + P<sub>2</sub>MS<sub>2</sub> + ... where
  - MS<sub>0</sub> is minimum sum obtained by setting P<sub>1</sub> = P<sub>2</sub> .. =0
  - MS<sub>1</sub> is minimum sum obtained by setting P<sub>1</sub> = 1, P<sub>j</sub> = 0 (j ≠ 1), and replacing all 1's on the map with don't cares.
- Previously, G = A'B' + ACD + EA'D + FAD.



$$X = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC$$




- Figure 4–35  
Example of mapping directly from a truth table to a Karnaugh map.

- Figure 4–36 Example of the use of “don’t care” conditions to simplify an expression.

Inputs <i>A B C D</i>	Output <i>Y</i>
0 0 0 0	0
0 0 0 1	0
0 0 1 0	0
0 0 1 1	0
0 1 0 0	0
0 1 0 1	0
0 1 1 0	0
0 1 1 1	1
1 0 0 0	1
1 0 0 1	1
1 0 1 0	X
1 0 1 1	X
1 1 0 0	X
1 1 0 1	X
1 1 1 0	X
1 1 1 1	X


(a) Truth table

Don't cares

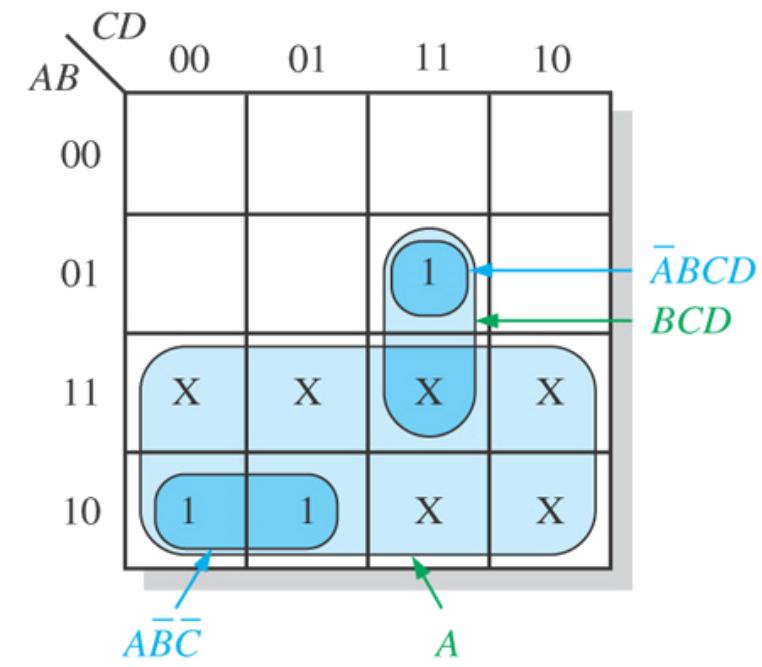

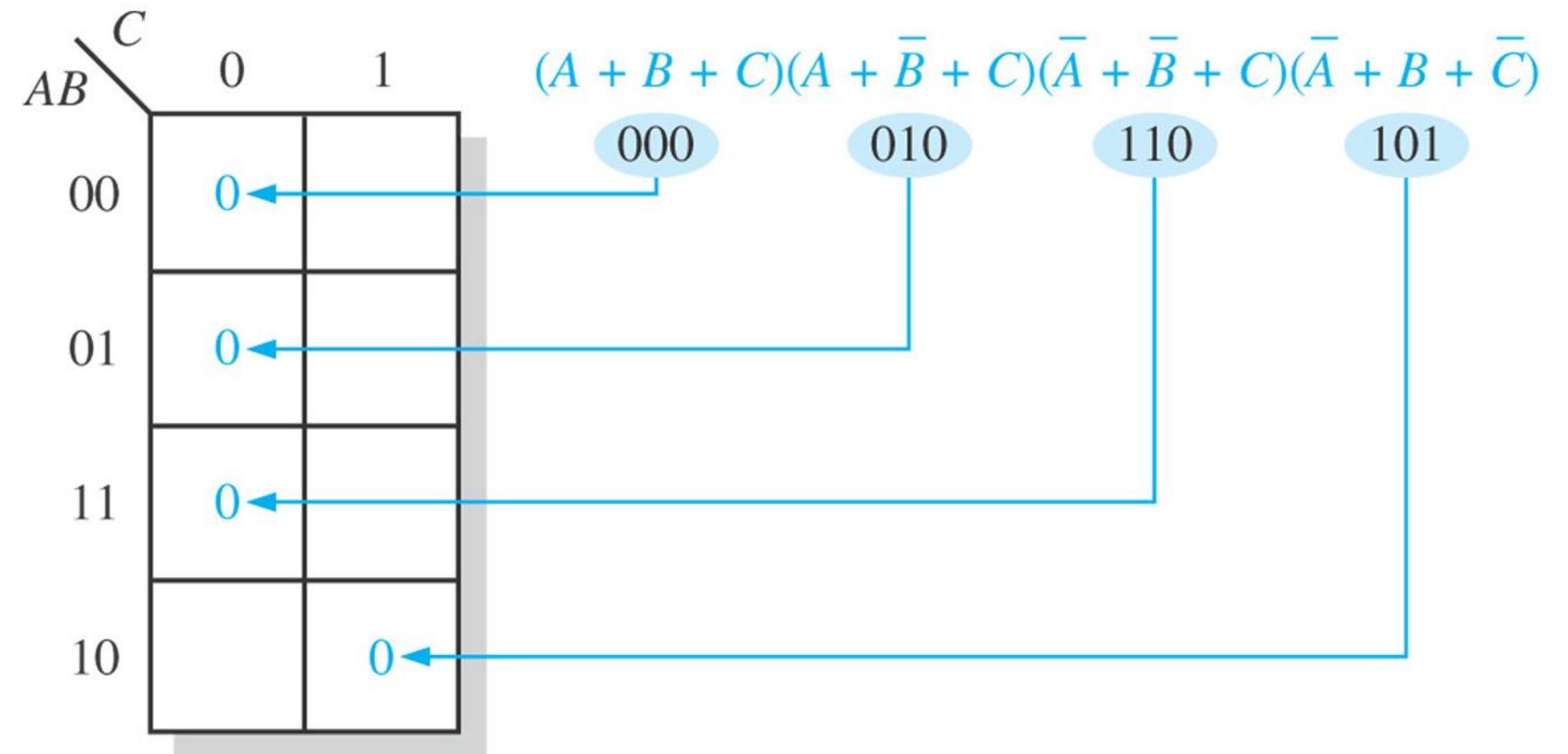(b) Without “don’t cares”  $Y = A\bar{B}\bar{C} + \bar{A}BCD$   
With “don’t cares”  $Y = A + BCD$

- Figure 4-37  
Example of mapping a standard POS expression.






Jiangxi University of Science and Technology


# Minimization
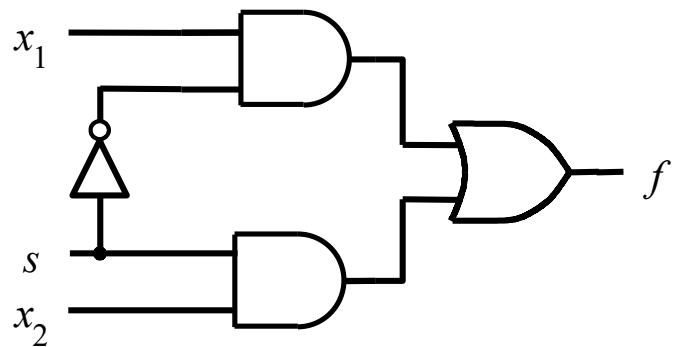
# Example: 2-1 Multiplexer (Definition)

- Has two inputs:  $x_1$  and  $x_2$
- Also has another input line  $s$
- If  $s=0$ , then the output is equal to  $x_1$
- If  $s=1$ , then the output is equal to  $x_2$



(b) Circuit

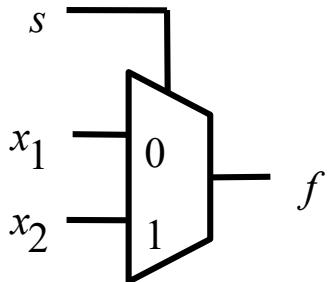


(c) Graphical symbol

# Truth Table for a 2-1 Multiplexer

Let's Draw the K-map


$s\ x_1\ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

$s\ x_1\ x_2$	$f(s, x_1, x_2)$
$m_0\ 0\ 0\ 0$	0
$m_1\ 0\ 0\ 1$	0
$m_2\ 0\ 1\ 0$	1
$m_3\ 0\ 1\ 1$	1
$m_4\ 1\ 0\ 0$	0
$m_5\ 1\ 0\ 1$	1
$m_6\ 1\ 1\ 0$	0
$m_7\ 1\ 1\ 1$	1

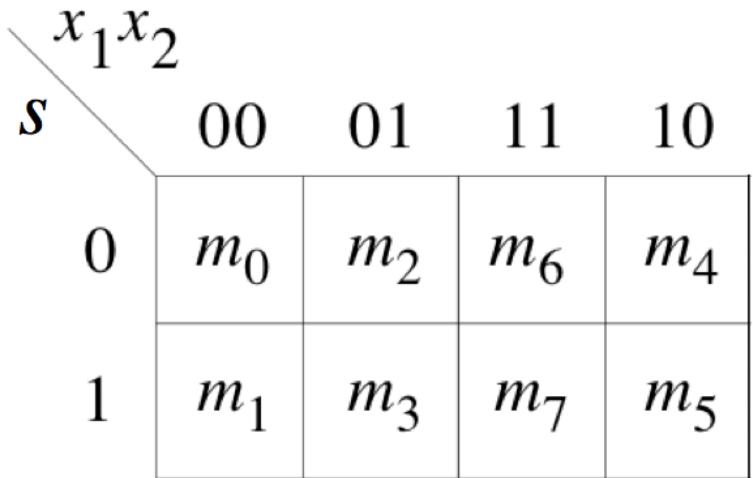


# Let's Draw the K-map


	$s$	$x_1$	$x_2$	$f(s, x_1, x_2)$
$m_0$	0	0	0	0
$m_1$	0	0	1	0
$m_2$	0	1	0	1
$m_3$	0	1	1	1
$m_4$	1	0	0	0
$m_5$	1	0	1	1
$m_6$	1	1	0	0
$m_7$	1	1	1	1

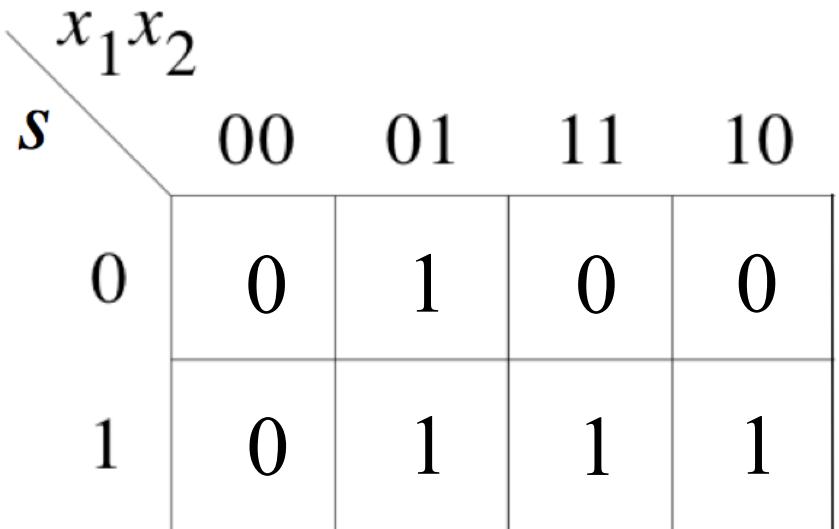

# Let's Draw the K-map

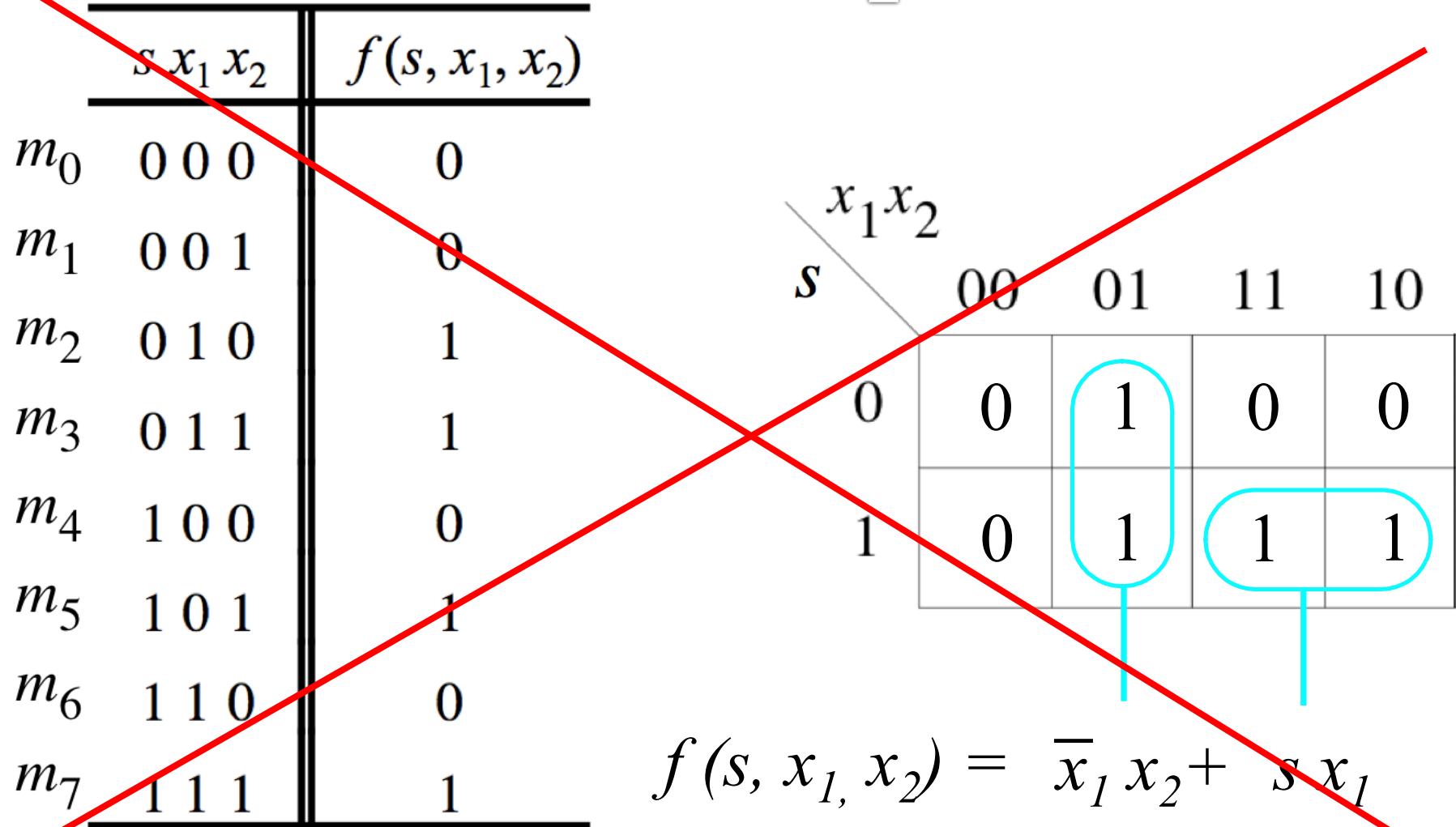

Something is wrong!

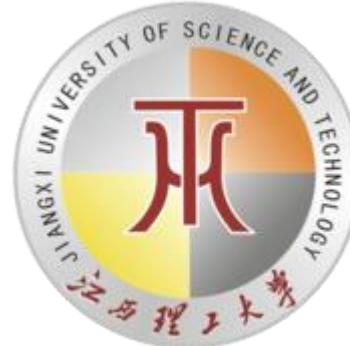

Jiangxi University of Science and Technology

Compare this with the  
SOP derivation

# Let's Derive the SOP form



$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Where should we put the negation signs?

$$\overline{s} x_1 \overline{x}_2$$

$$\overline{s} x_1 x_2$$

$$s \overline{x}_1 x_2$$

$$s x_1 x_2$$

$$f(s, x_1, x_2) = \overline{s} x_1 \overline{x}_2 + \overline{s} x_1 x_2 + s \overline{x}_1 x_2 + s x_1 x_2$$



# Let's simplify this expression


$$f(s, x_1, x_2) = \bar{s}x_1\bar{x}_2 + \bar{s}x_1x_2 + s\bar{x}_1x_2 + sx_1x_2$$

$$f(s, x_1, x_2) = \bar{s}x_1(\bar{x}_2 + x_2) + s(\bar{x}_1 + x_1)x_2$$

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$

# Let's Draw the K-map again


$s\ x_1\ x_2$	$f(s, x_1, x_2)$
$m_0\ 0\ 0\ 0$	0
$m_1\ 0\ 0\ 1$	0
$m_2\ 0\ 1\ 0$	1
$m_3\ 0\ 1\ 1$	1
$m_4\ 1\ 0\ 0$	0
$m_5\ 1\ 0\ 1$	1
$m_6\ 1\ 1\ 0$	0
$m_7\ 1\ 1\ 1$	1

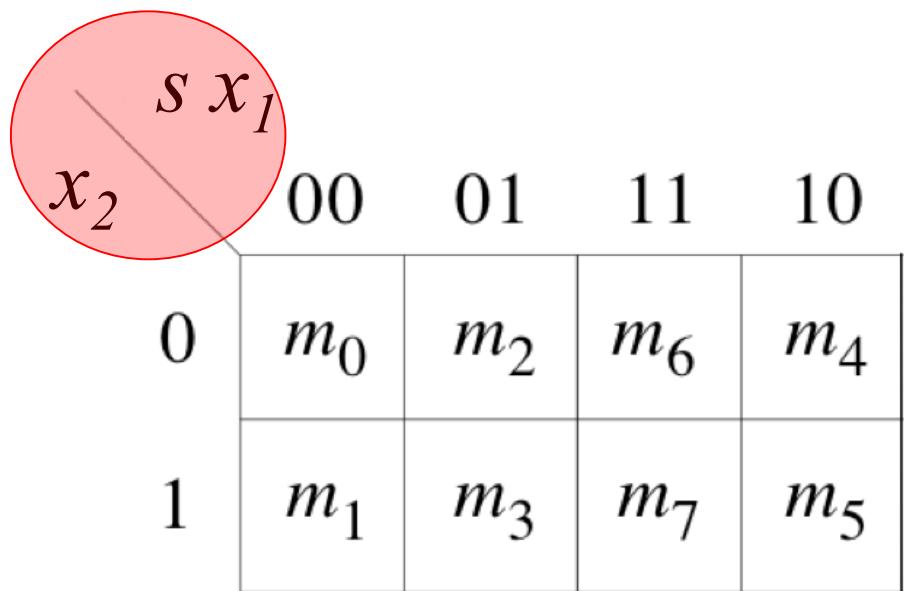

The order of the labeling matters.

# Let's Draw the K-map again

	$s$	$x_1$	$x_2$	$f(s, x_1, x_2)$
$m_0$	0	0	0	0
$m_1$	0	0	1	0
$m_2$	0	1	0	1
$m_3$	0	1	1	1
$m_4$	1	0	0	0
$m_5$	1	0	1	1
$m_6$	1	1	0	0
$m_7$	1	1	1	1

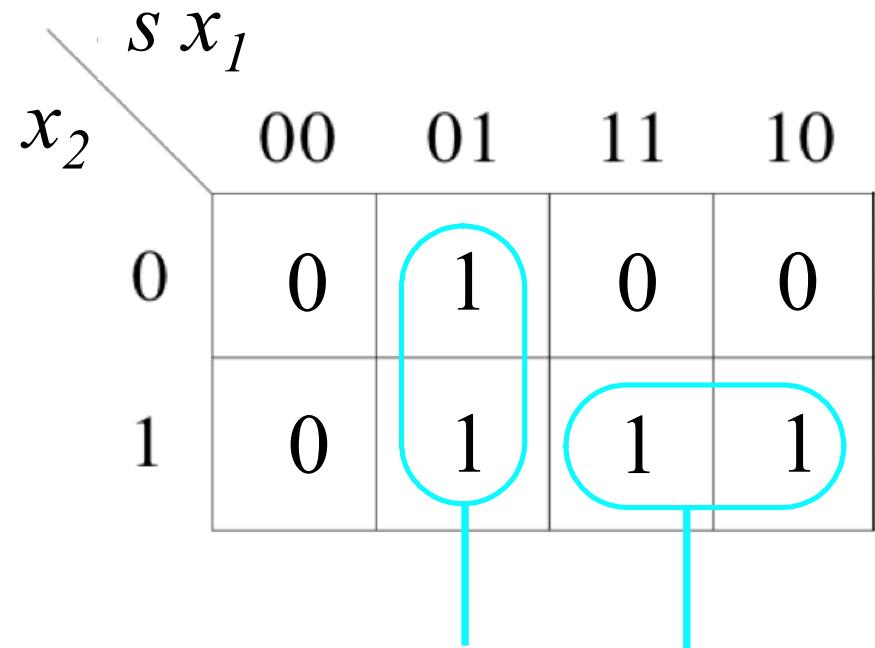

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$


This is correct!

# Two Different Ways to Draw the K-map




$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
<hr/>			
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

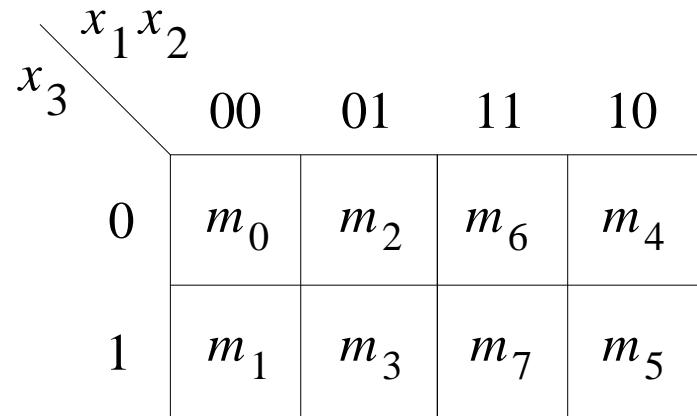

(b) Karnaugh map

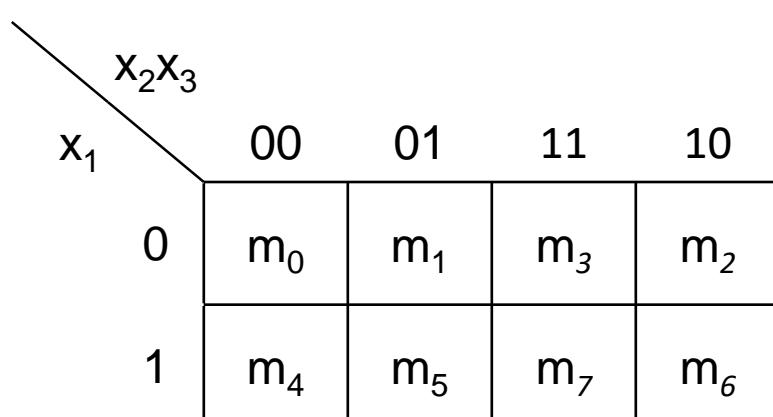


# Another Way to Draw 3-variable K-map




$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

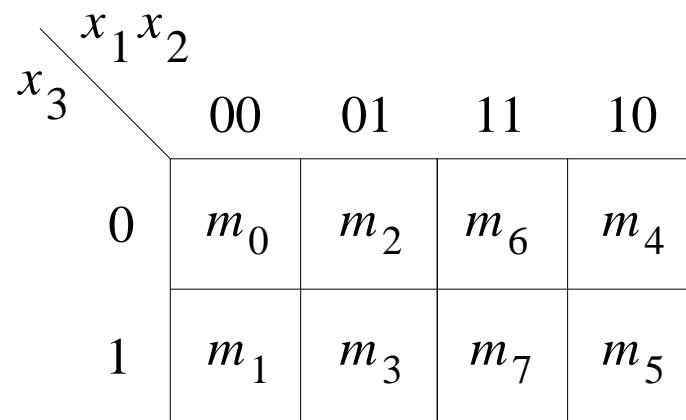

(b) Karnaugh map

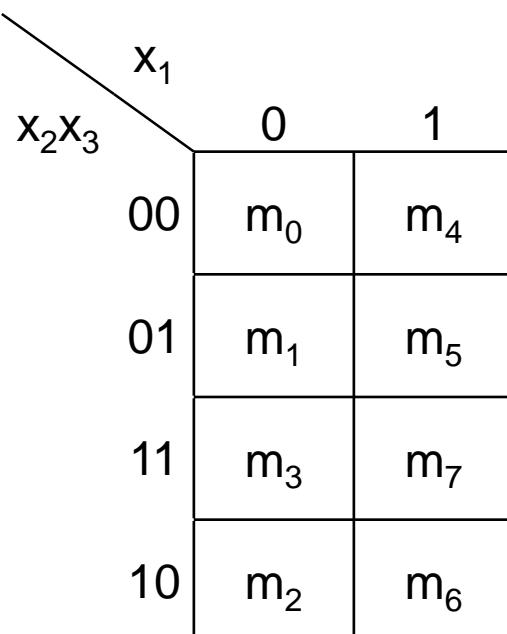



# Gray Code

- Sequence of binary codes
- Neighboring lines vary by only 1 bit

00	000
01	001
11	011
10	010
	110
	111
	101
	100

# Gray Code & K-map



	$s$	$x_1$	$x_2$
$m_0$		0 0 0	
$m_1$		0 0 1	
$m_2$		0 1 0	
$m_3$		0 1 1	
$m_4$		1 0 0	
$m_5$		1 0 1	
$m_6$		1 1 0	
$m_7$		1 1 1	

$s \backslash x_1$


$x_2$	00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

$s \backslash x_1$

$x_2$	00	01	11	10
0	000	010	110	100
1	001	011	111	101

# Gray Code & K-map


	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

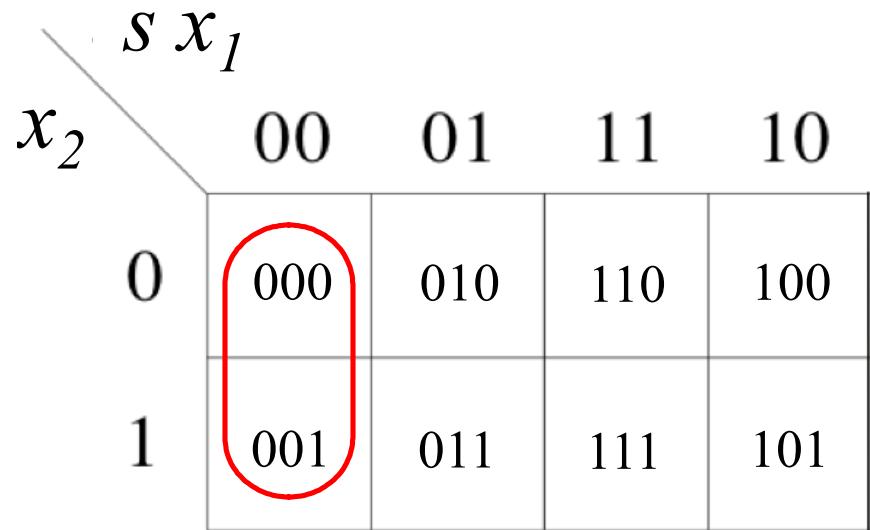

These two neighbors  
differ only in the LAST bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

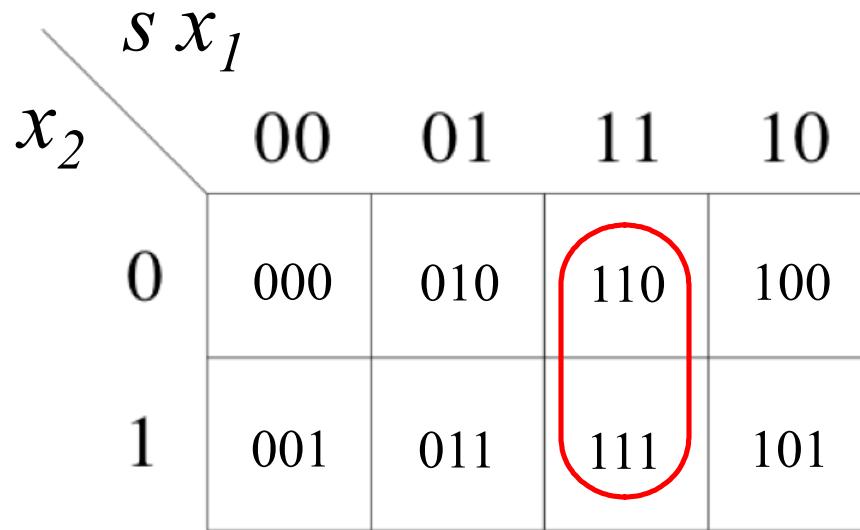


These two neighbors  
differ only in the LAST bit



# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

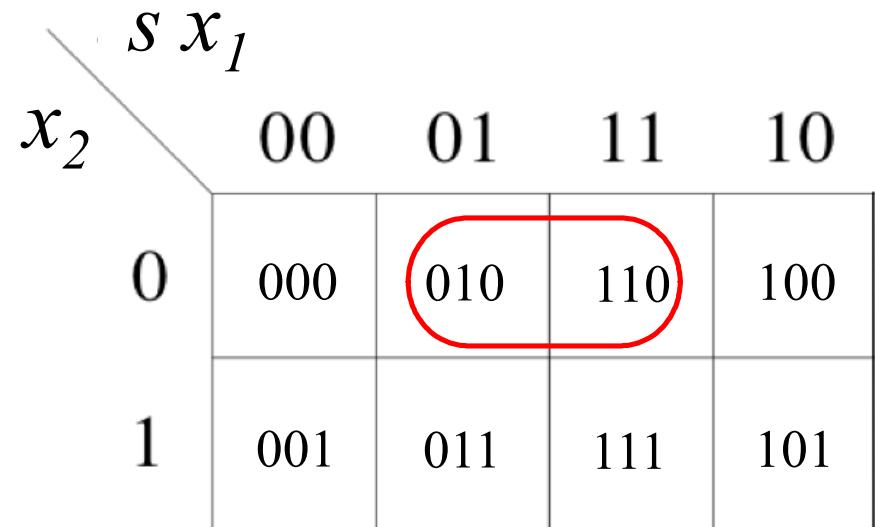


These two neighbors  
differ only in the FIRST bit



# Gray Code & K-map


	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

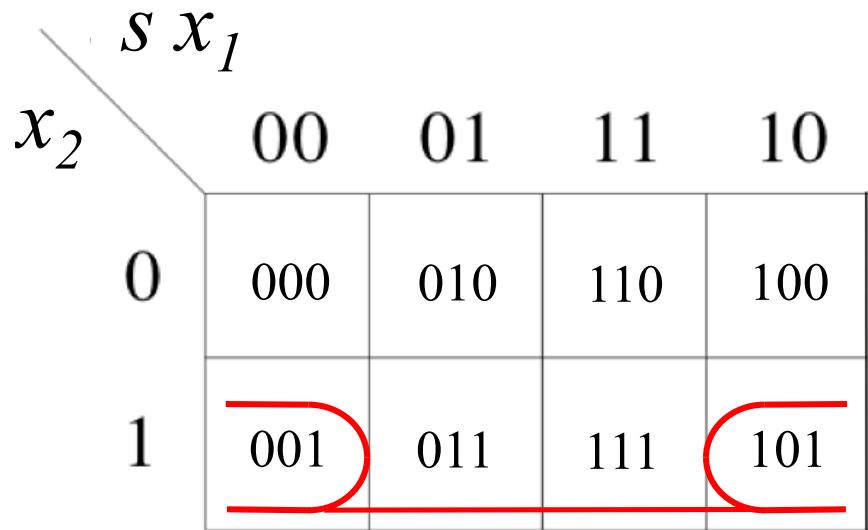

These two neighbors  
differ only in the FIRST bit

# Adjacency Rules


		$x_1$	$x_2$	$s$		
		00	01	11		
		0	000	010	110	100
		1	001	011	111	101

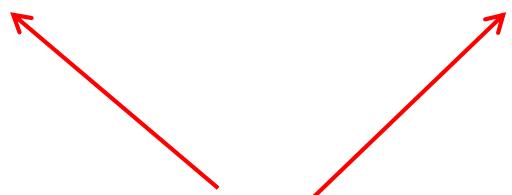

adjacent  
columns

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

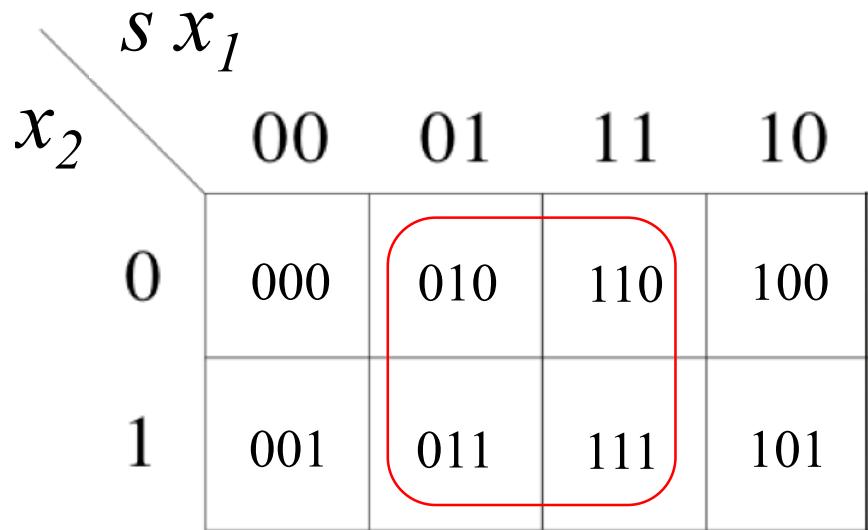


These four neighbors  
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

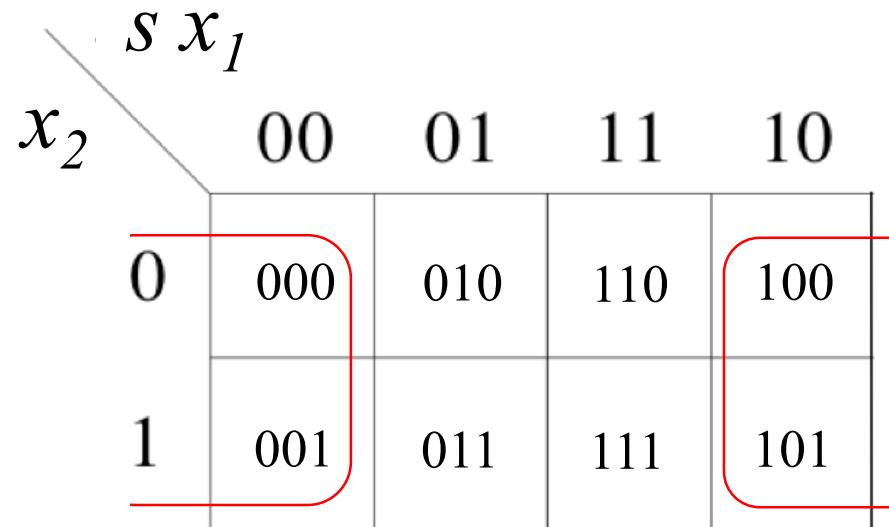


These four neighbors  
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit




# A four-variable Karnaugh map

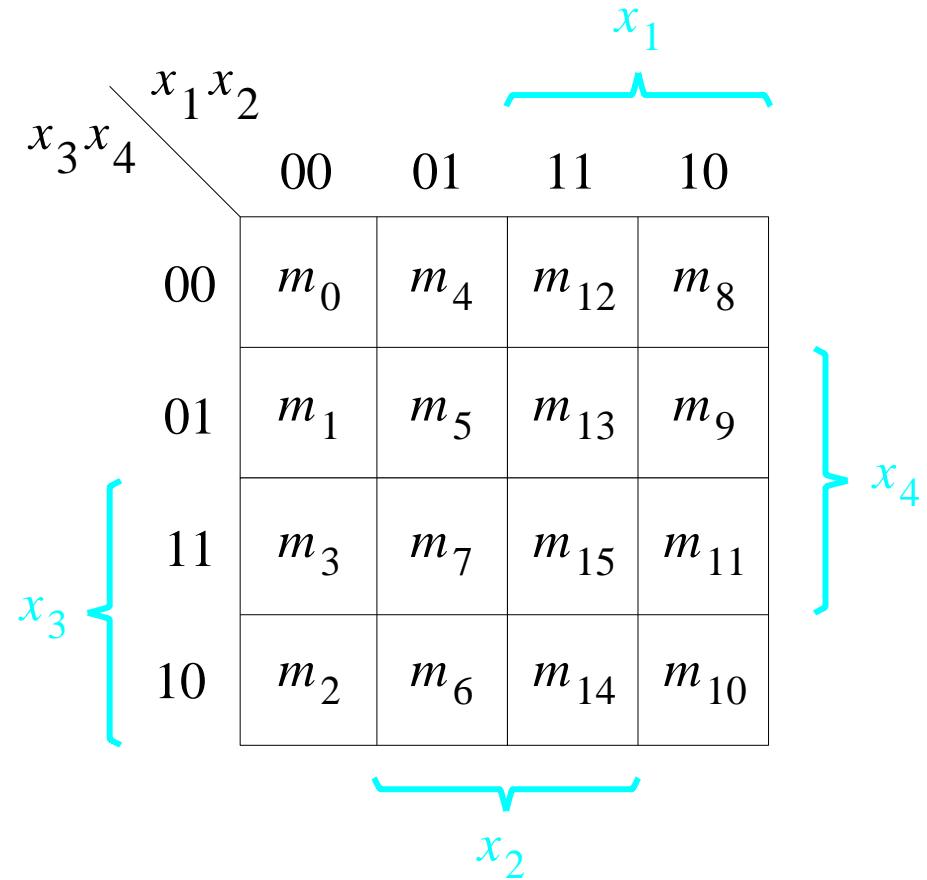



# A four-variable Karnaugh map

$x_1$	$x_2$	$x_3$	$x_4$	
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

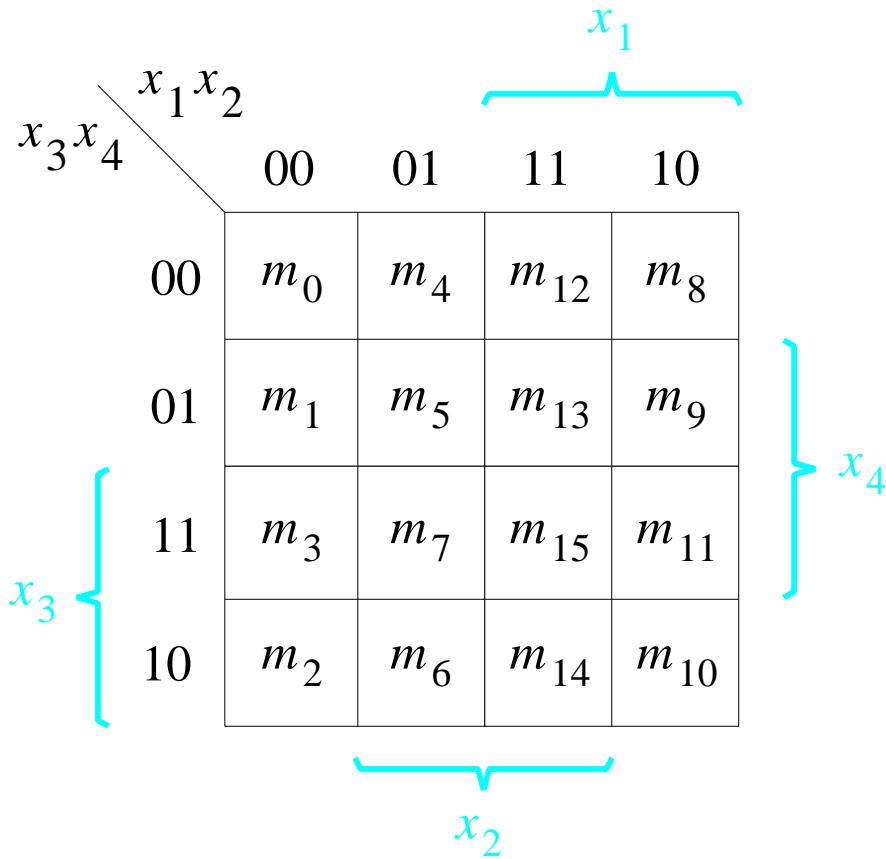

# Adjacency Rules

		$x_1x_2$	$x_1x_2$	$x_1x_2$	$x_1x_2$
		00	01	11	10
0		$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$	

adjacent columns

		$x_1x_2$	$x_1x_2$	$x_1x_2$	$x_1x_2$
		00	01	11	10
00		$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$	
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$	
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$	


adjacent rows

adjacent columns

# Adjacency Rules

		$x_1x_2$	$x_3$			
		00	01	11	10	
		0	$m_0$	$m_2$	$m_6$	$m_4$
		1	$m_1$	$m_3$	$m_7$	$m_5$

adjacent  
columns

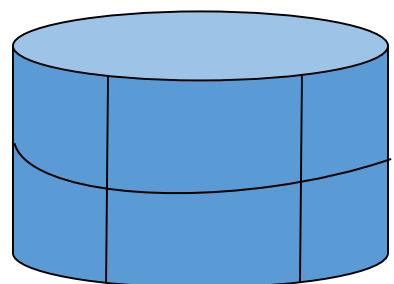


As if the K-map were  
drawn on a cylinder

# Adjacency Rules



		$x_1x_2$	$x_3$
		00	01
0	0	$m_0$	$m_2$
1	0	$m_1$	$m_3$
		11	10
1	1	$m_7$	$m_5$

adjacent columns

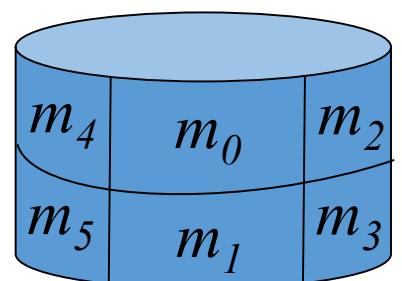

As if the K-map were drawn on a cylinder

# Adjacency Rules

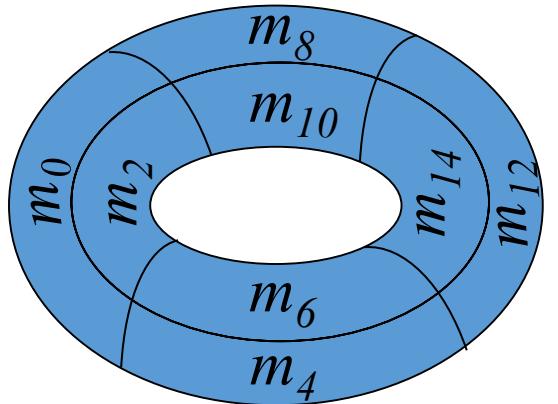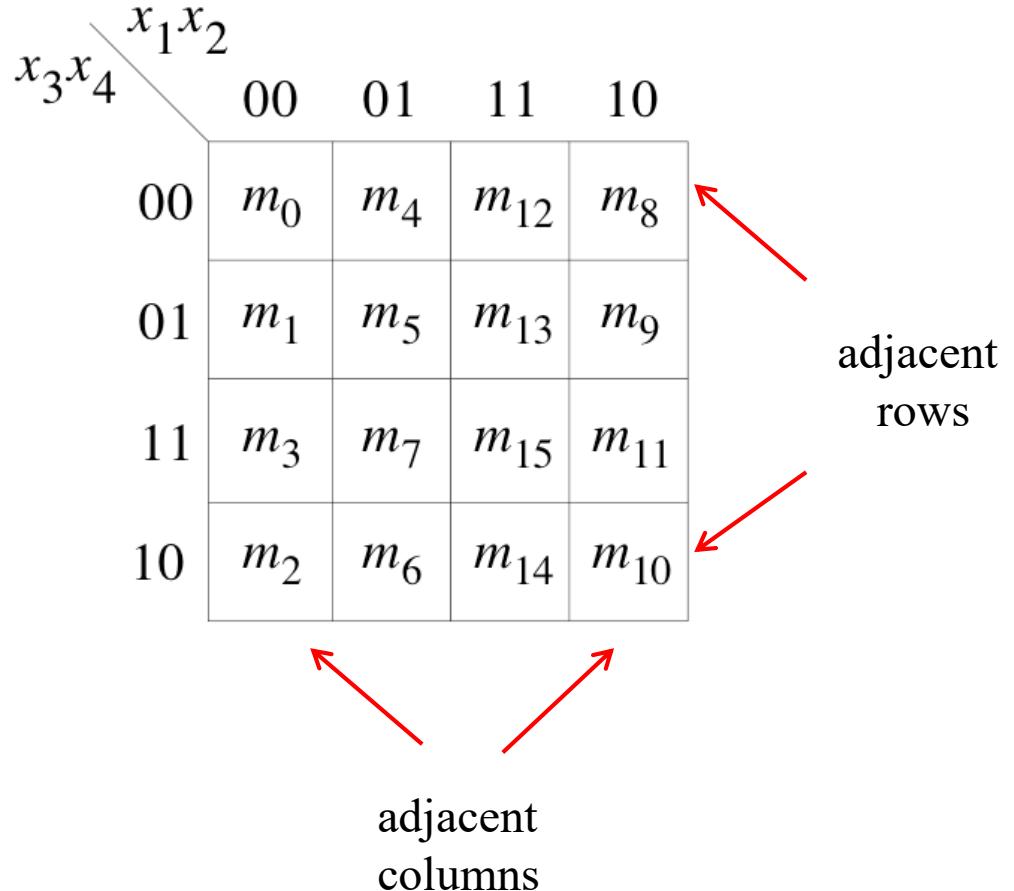


As if the K-map were drawn on a torus

# Gray Code & K-map




$x_1$	$x_2$	$x_3$	$x_4$	
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

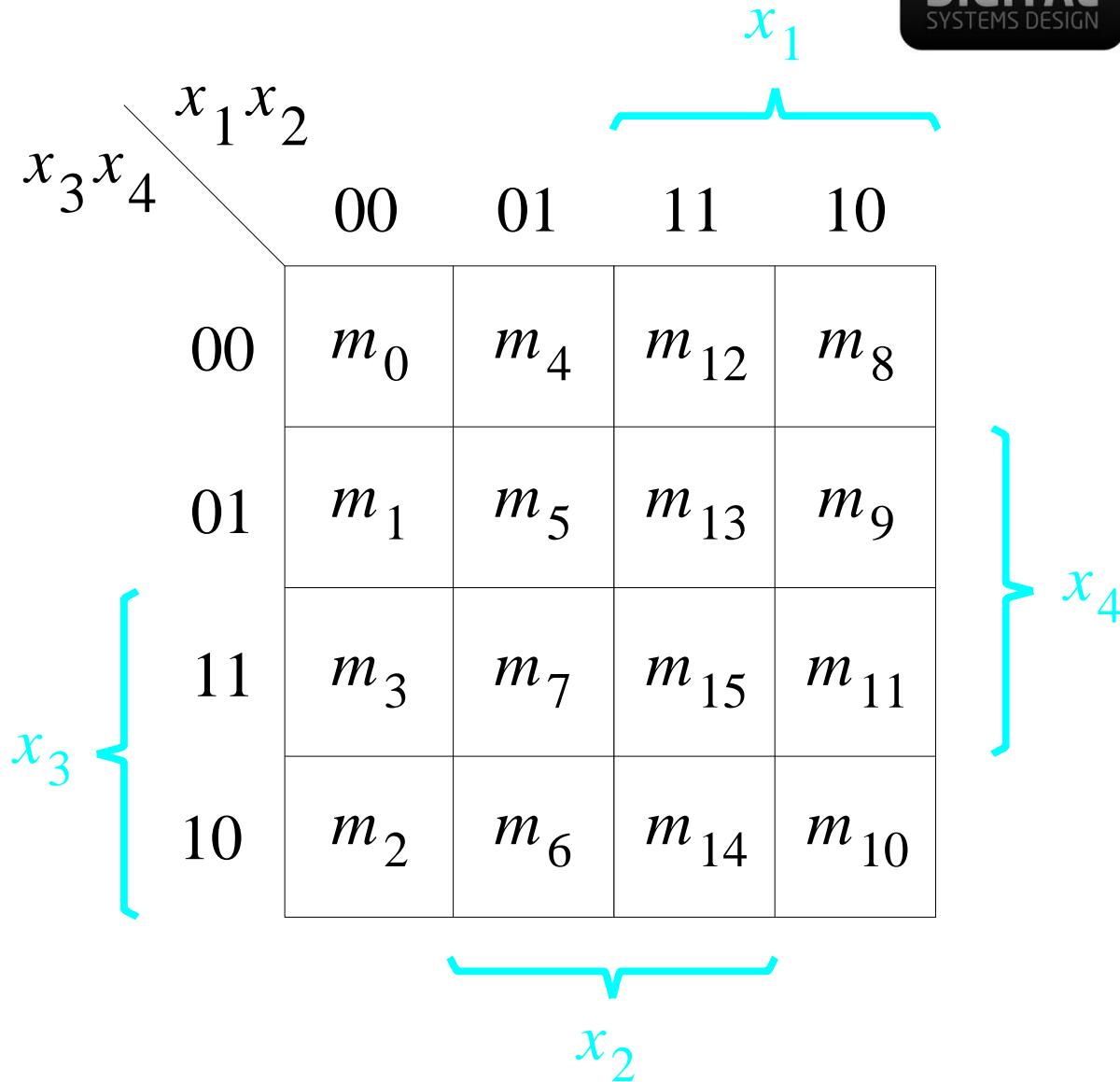



# Gray Code & K-map



$x_1$	$x_2$	$x_3$	$x_4$	
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

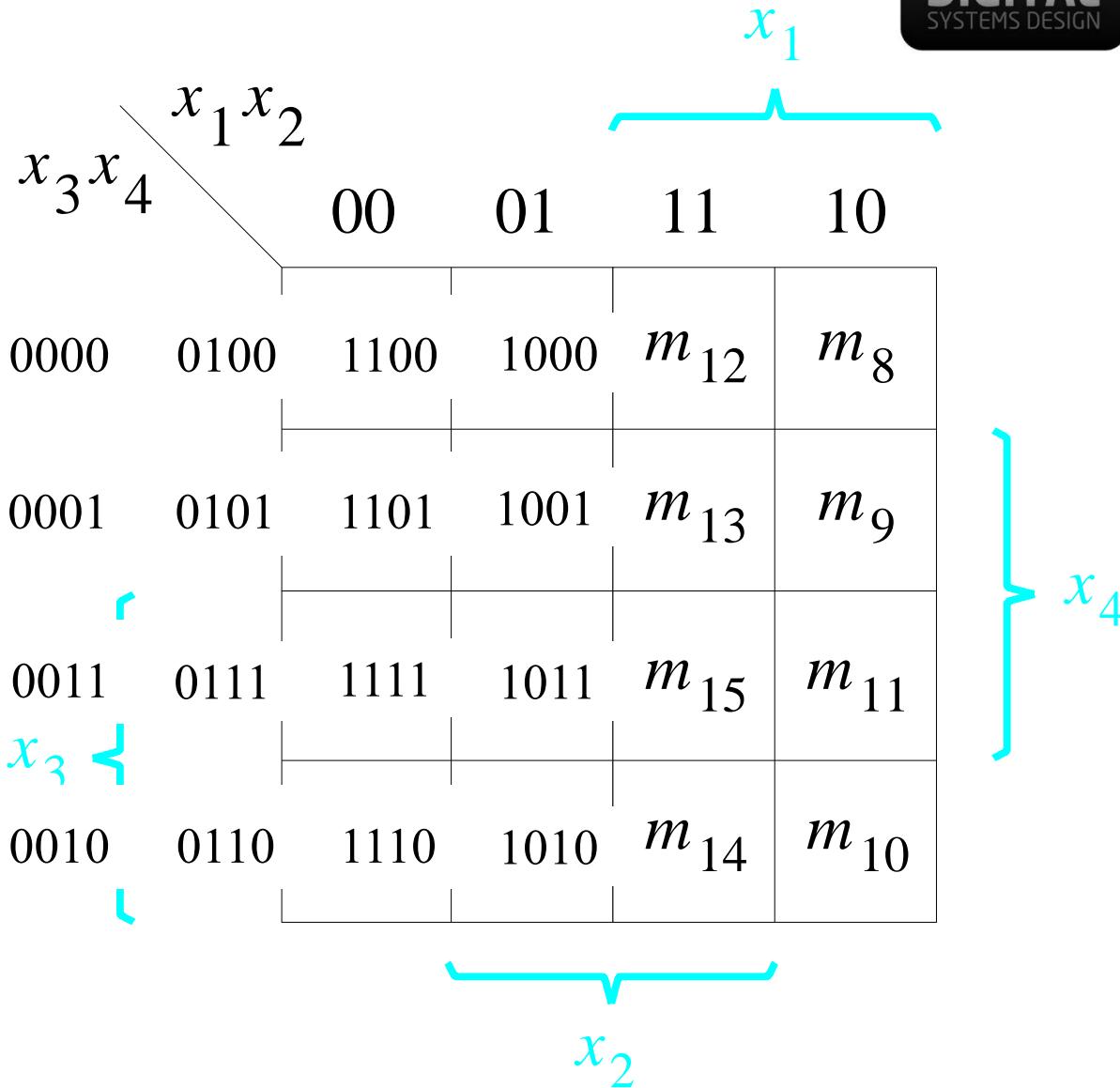
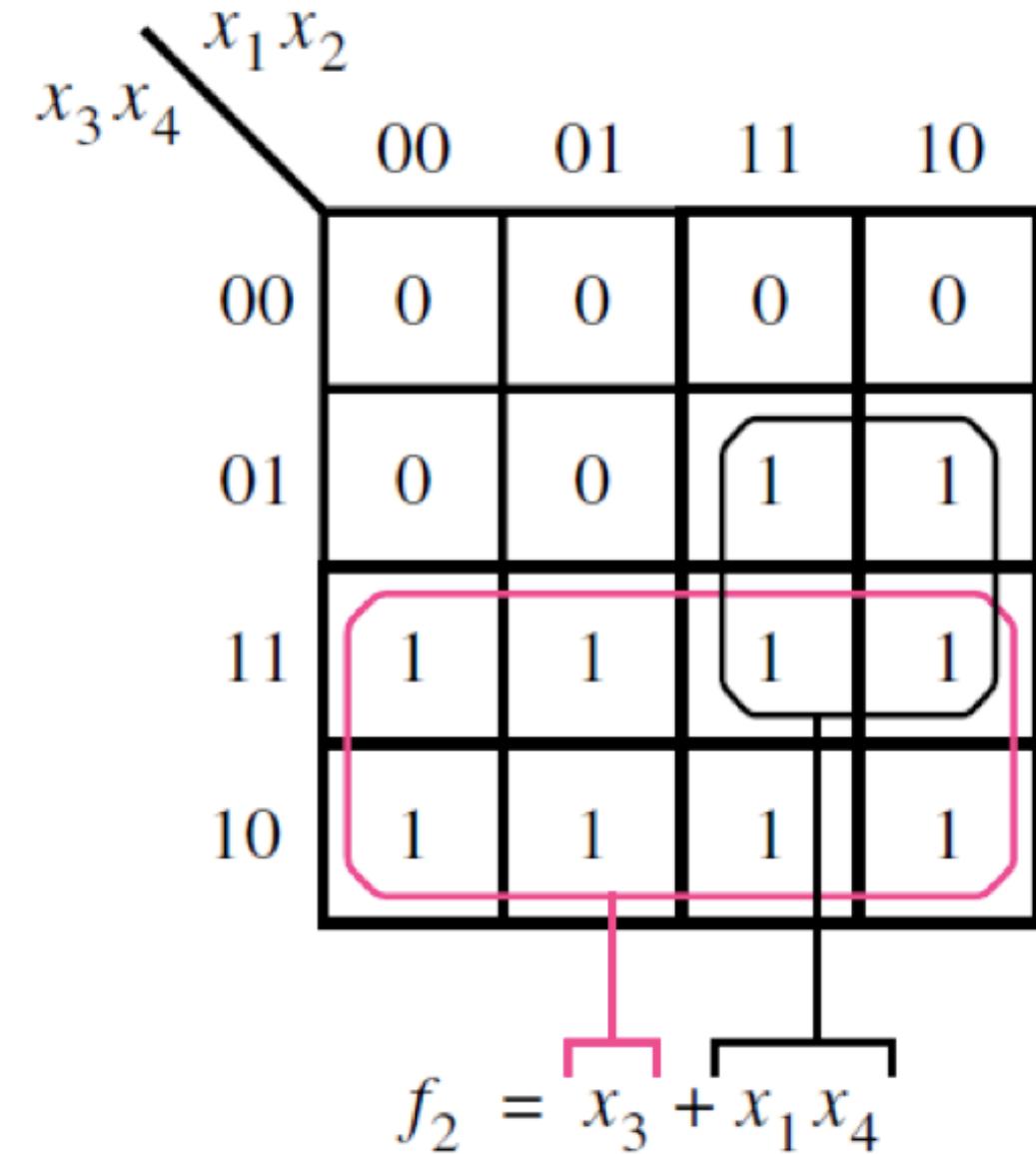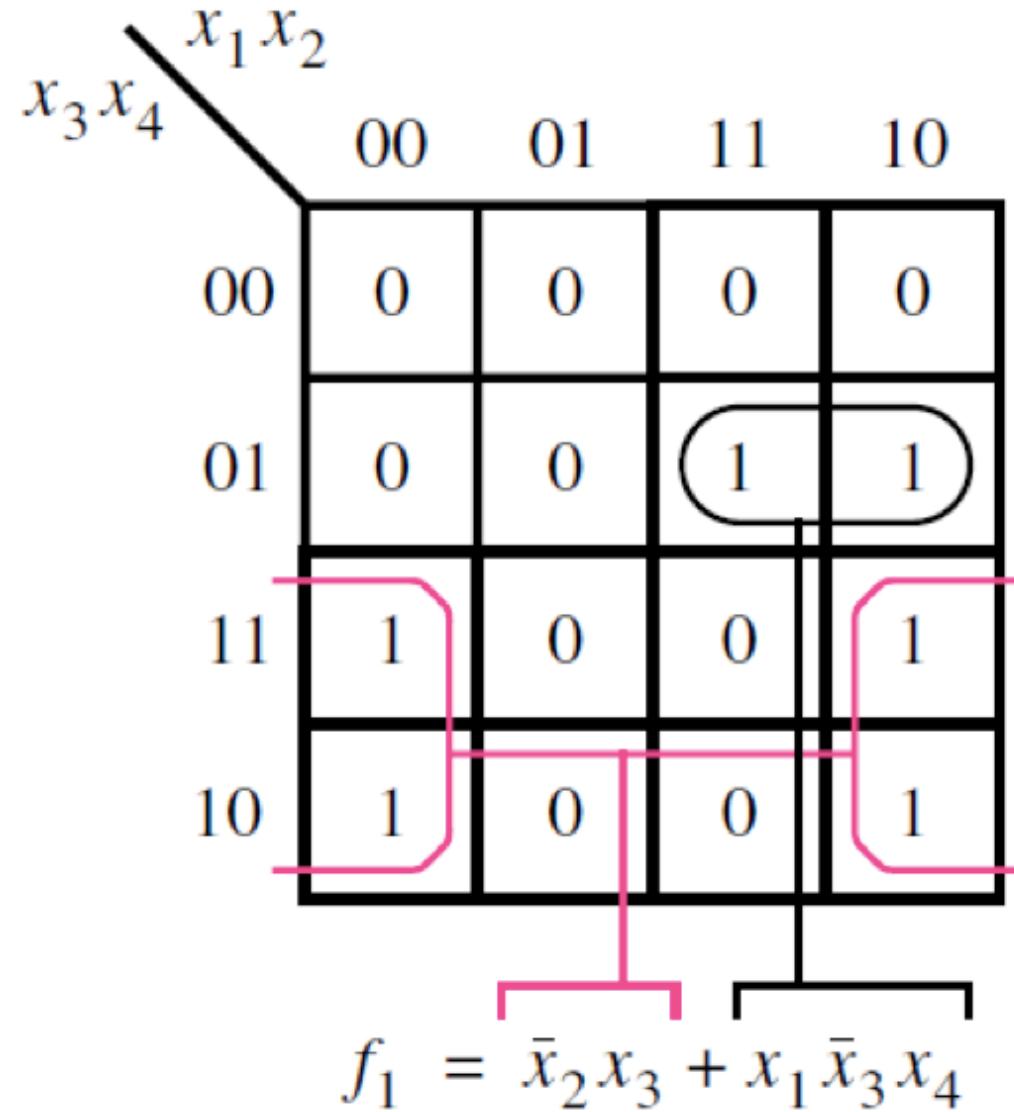
# Example of a four-variable Karnaugh map





Jiangxi University of Science and Technology

# Strategy For Minimization

# Grouping Rules



- Group “1”s with rectangles
- Both sides a power of 2:
  - 1x1, 1x2, 2x1, 2x2, 1x4, 4x1, 2x4, 4x2, 4x4
- Can use the same minterm more than once
- Can wrap around the edges of the map
- Some rules in selecting groups:
  - Try to use as few groups as possible to cover all “1”s.
  - For each group, try to make it as large as you can (i.e., if you can use a 2x2, don’t use a 2x1 even if that is enough).



# Terminology

Literal: a variable, complemented or uncomplemented

Some Examples:

- $X_1$
- $X_2$

# Terminology

- Implicant: product term that indicates the input combinations for which the function output is 1
- Example

- $\bar{x}_1$  - indicates that  $\bar{x}_1\bar{x}_2$  and  $\bar{x}_1x_2$  yield output of 1

	$x_1$	0	1
$x_2$	0	1	0
1	1	0	

# Terminology

- Prime Implicant
  - Implicant that cannot be combined into another implicant with fewer literals
  - Some Examples

		$x_1x_2$				
		$x_3$	00	01	11	10
$x_3$	0	0	1	1	1	1
	1	1	1	1	0	

Not prime

		$x_1x_2$				
		$x_3$	00	01	11	10
$x_3$	0	0	1	1	1	1
	1	1	1	1	1	0

Prime



# Terminology

- Essential Prime Implicant
  - Prime implicant that includes a minterm not covered by any other prime implicant
  - Some Examples

		$x_1x_2$		
		$x_3$	00	01
$x_3$	0	0	1	1
	1	1	1	0

# Terminology

- Cover
  - Collection of implicants that account for all possible input valuations where output is 1
  - Ex.  $x_1'x_2x_3 + x_1x_2x_3' + x_1x_2'x_3'$
  - Ex.  $x_1'x_2x_3 + x_1x_3'$

		$x_1x_2$		
		$x_3$	00	01
$x_3$	0	0	0	1
	1	0	1	0


# Example

- Give the Number of
  - Implicants?
  - Prime Implicants?
  - Essential Prime Implicants?



		$x_1x_2$		
		00	01	11
		10		
$x_3$	0	1	1	0
	1	1	1	1
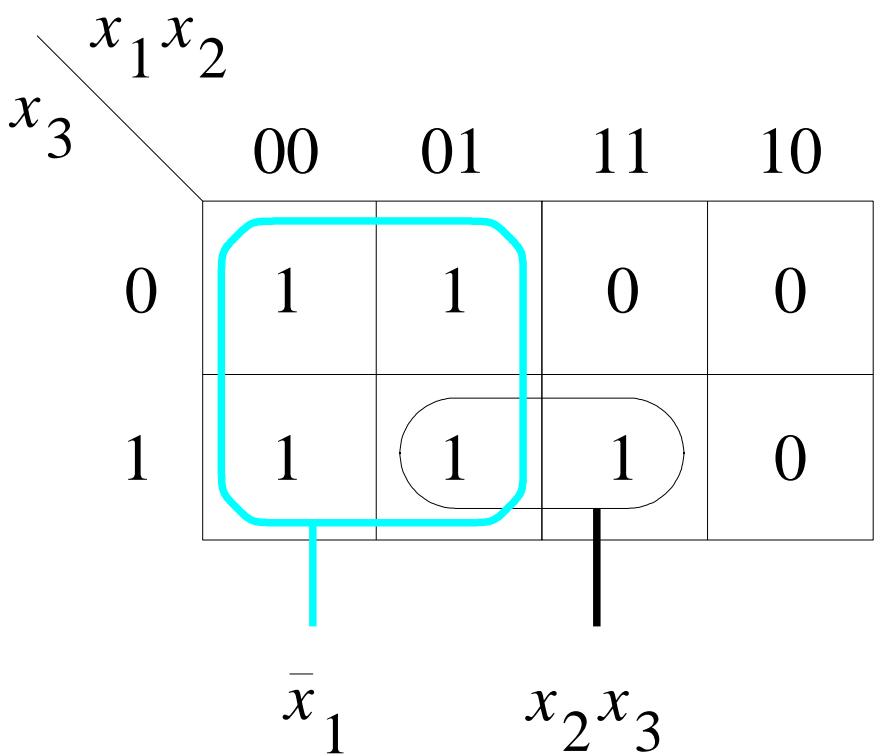
# Example

Three-variable function  $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$




# Example

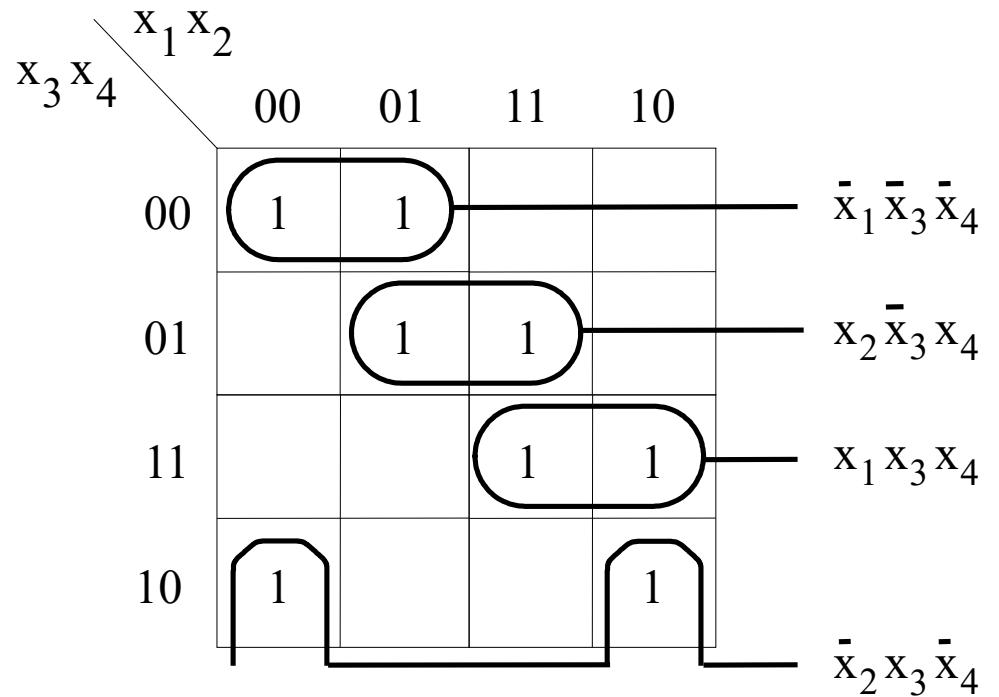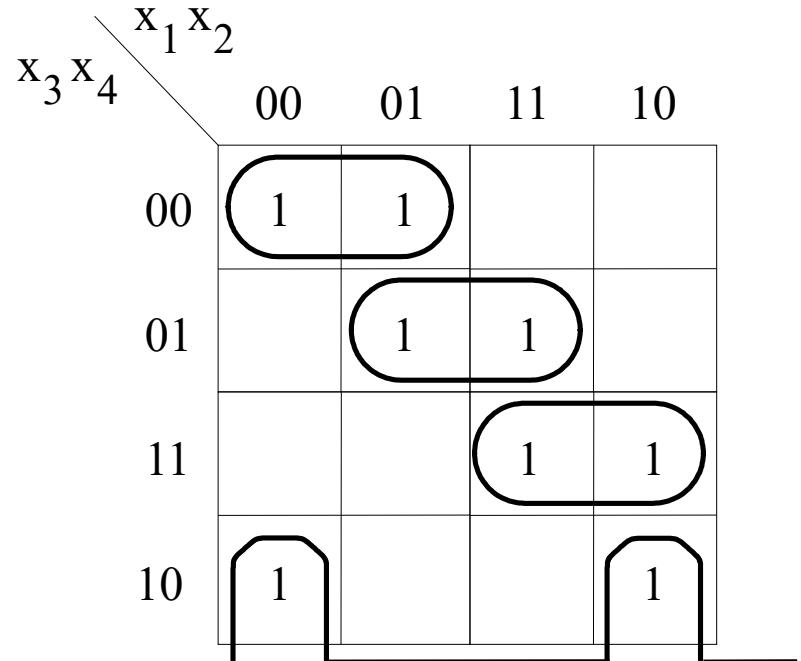


$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$

# Example: Another Solution

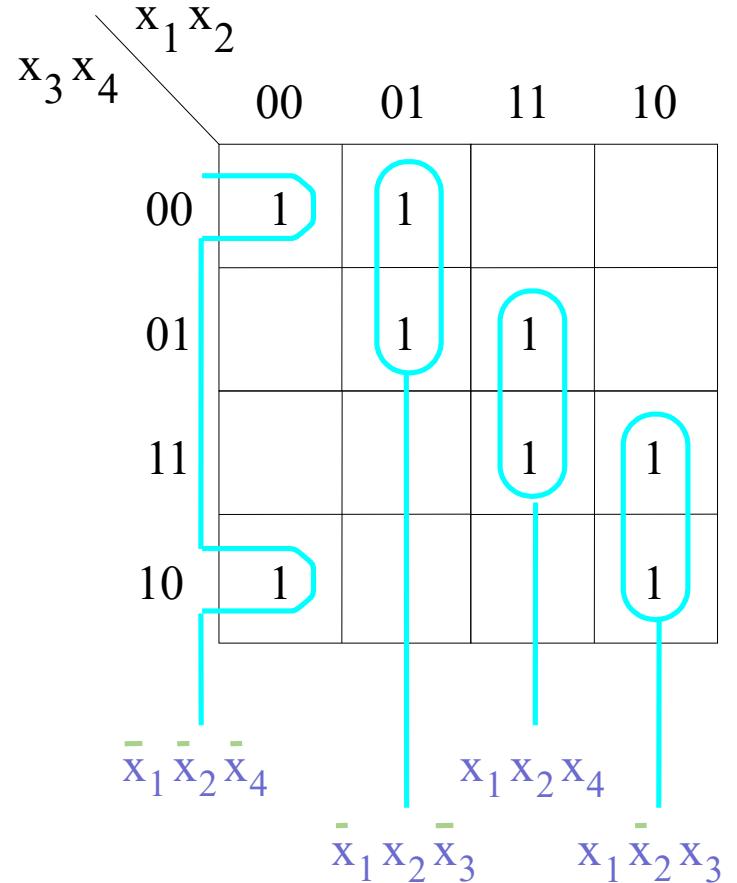


$$f = \overline{x_1} \overline{x_2} \overline{x_4} + \overline{x_1} x_2 \overline{x_3} + x_1 x_2 x_4 + x_1 \overline{x_2} x_3$$

# Example: Both Are Valid Solutions

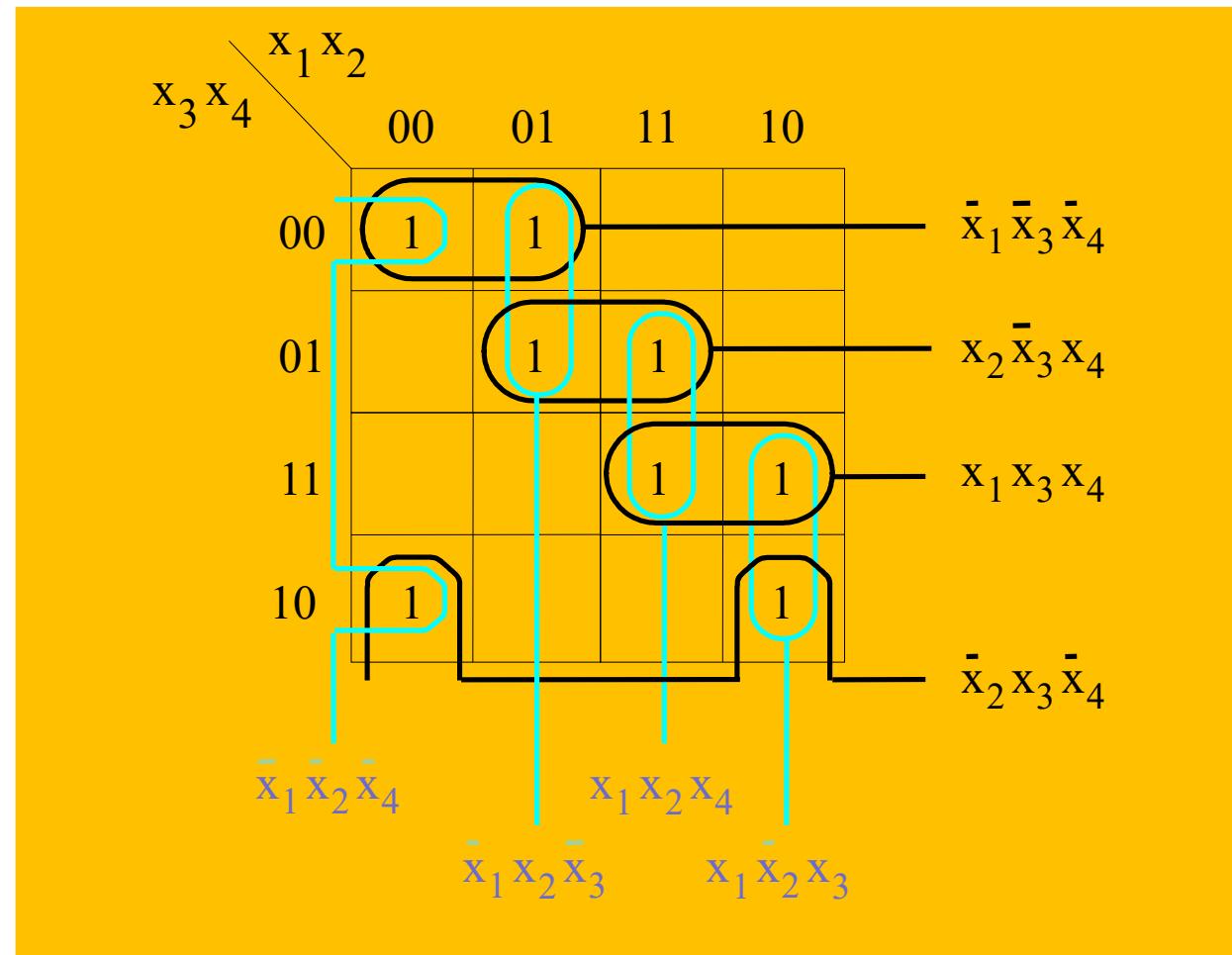

# Example: Both Are Valid Solutions

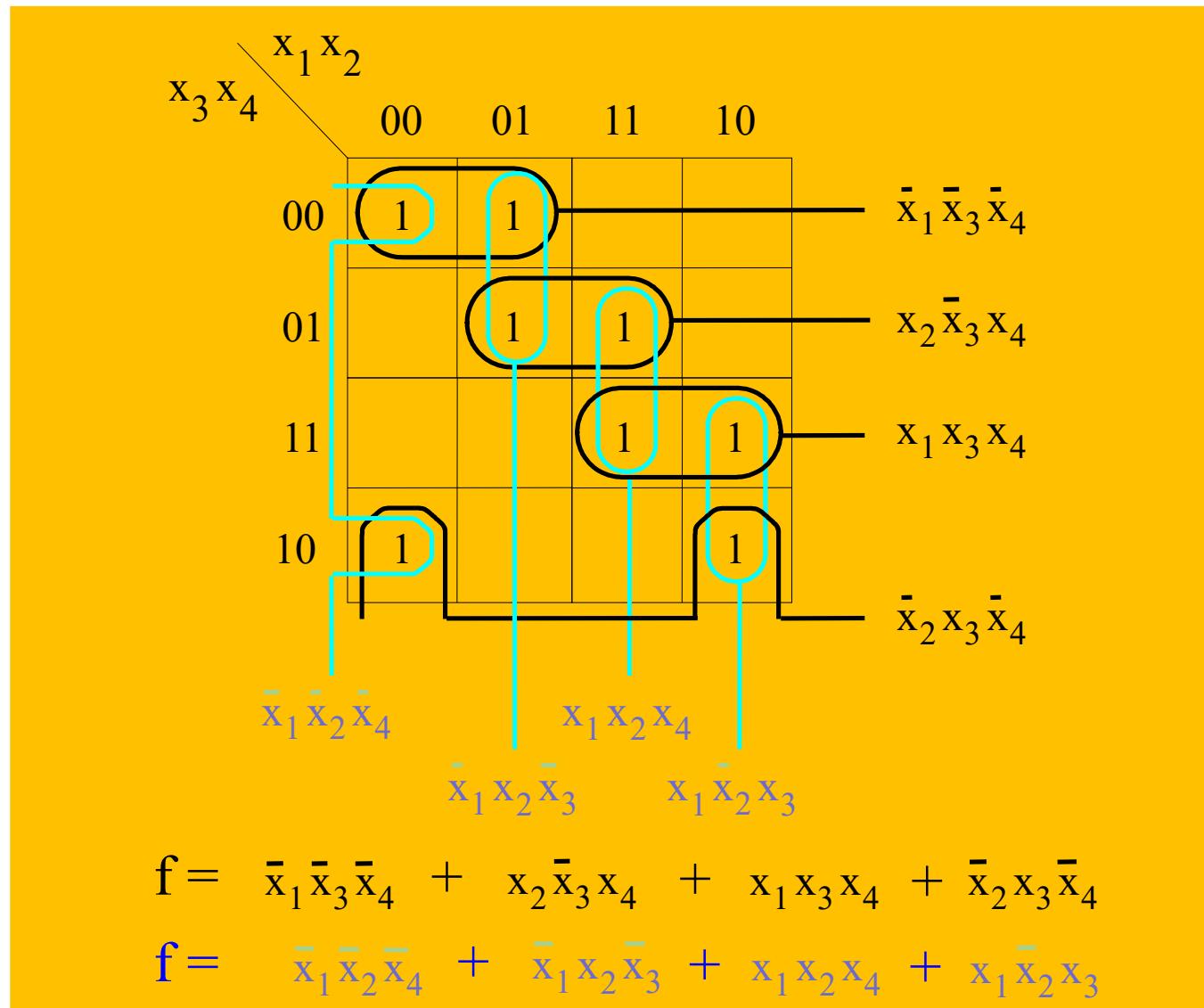



# Minimization of Product-of-Sums Forms




# Do You Still Remember This Boolean Algebra Theorem?

14a.  $x \cdot y + x \cdot \bar{y} = x$       **Combining**

14b.  $(x + y) \cdot (x + \bar{y}) = x$

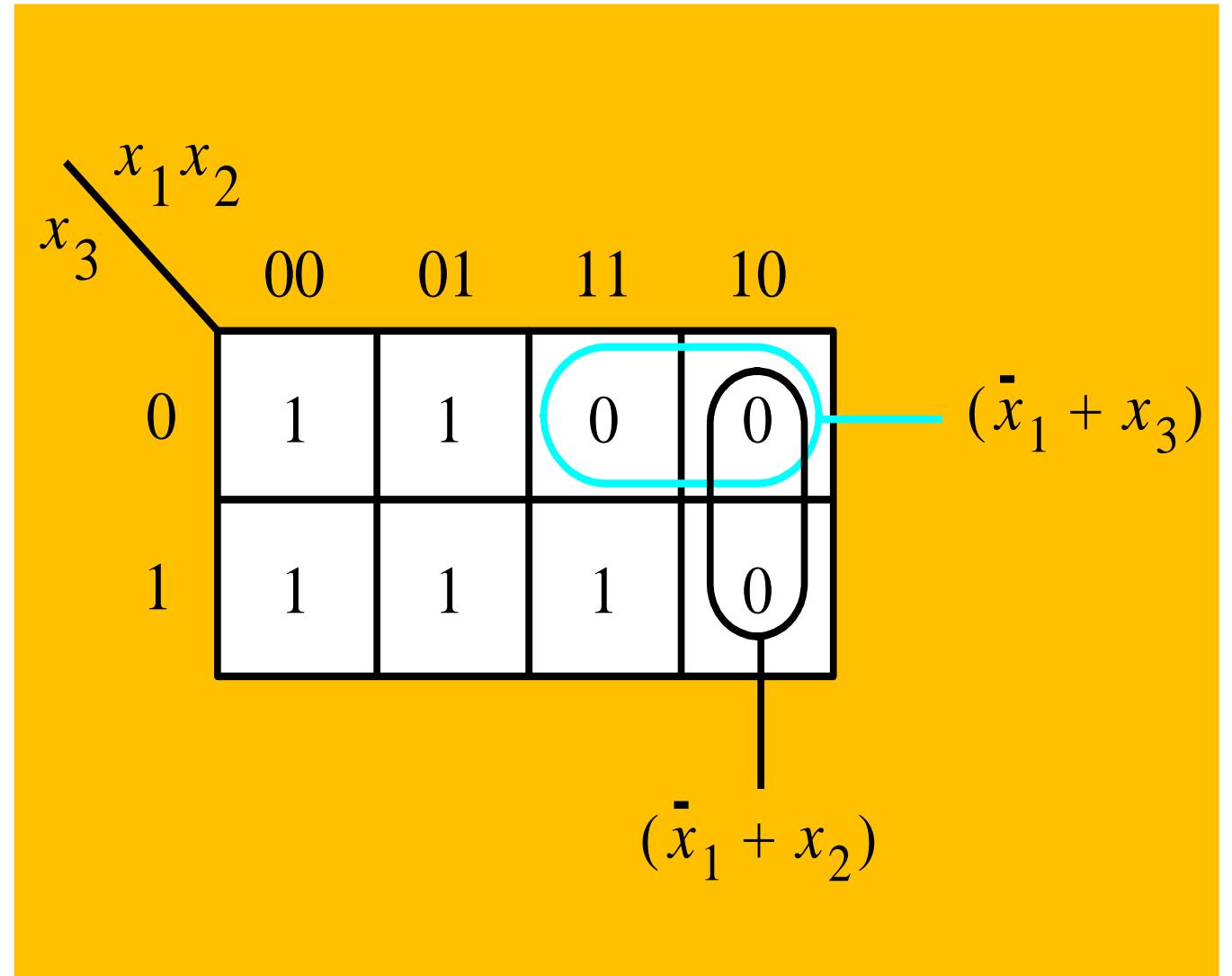**POS minimization of  $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$**



**POS minimization of  $f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$**

$x_1 x_2$	00	01	11	10
$x_3 x_4$	00	0	0	0
	01	0	1	1
	11	1	1	0
	10	1	1	1

Diagram illustrating the POS minimization of the function  $f(x_1, \dots, x_4) = \prod M(0, 1, 4, 8, 9, 12, 15)$ . The Karnaugh map shows the function values (0 or 1) for all combinations of  $x_1, x_2, x_3, x_4$ . The terms identified are:

- $(x_3 + x_4)$  covers minterms 0000, 0001, 0010, and 0100.
- $(x_2 + x_3)$  covers minterms 0001, 0010, 0100, and 0101.
- $(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$  covers minterm 0101.

The Karnaugh map is a 4x4 grid where rows represent  $x_1 x_2$  and columns represent  $x_3 x_4$ . The columns are labeled 00, 01, 11, 10 from left to right. The rows are labeled 00, 01, 11, 10 from top to bottom. The map shows the following values:

$x_1 x_2$	00	01	11	10
$x_3 x_4$	00	0	0	0
	01	0	1	1
	11	1	1	0
	10	1	1	1

Red circles highlight the minterms 0000, 0010, 0100, 0101, and 0101. Red lines group the minterms for the terms  $(x_3 + x_4)$ ,  $(x_2 + x_3)$ , and  $(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$ .

# Reference

- <http://www.ee.surrey.ac.uk/Projects/CAL/digital-logic/gatesfunc/>
- *CprE 281: Digital Logic, Iowa State University, Ames, IA, Copyright © Alexander Stoytchev*
- **Digital Systems: Principles and Applications, 11/e**
- *Ronald J. Tocci, Neal S. Widmer, Gregory L. Moss*

