



江西理工大学
Jiangxi University of Science and Technology
信息工程学院
School of information engineering



Dr Ata Jahangir Moshayedi



Clip Lecture series

Digital System Design

Spring_2020



Prof Associate , School of information engineering Jiangxi university of science and technology, China

EMAIL: ajm@jxust.edu.cn



Jiangxi University of Science and Technology

Sequential circuits




3 example with detail solution

Example 1




Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,

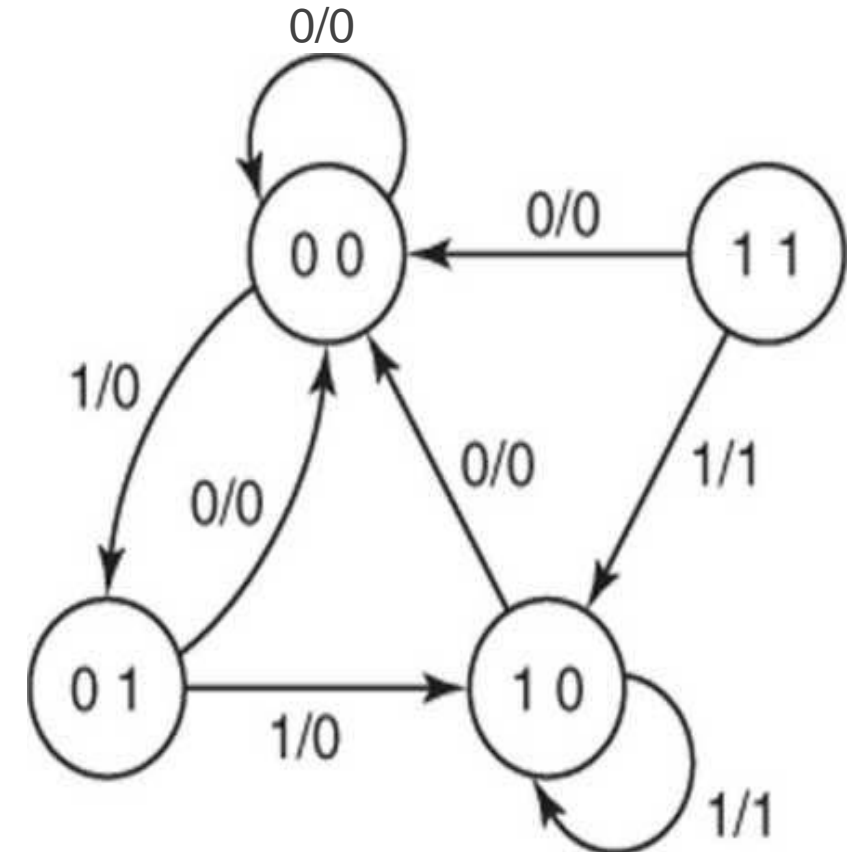

Example 1


Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,

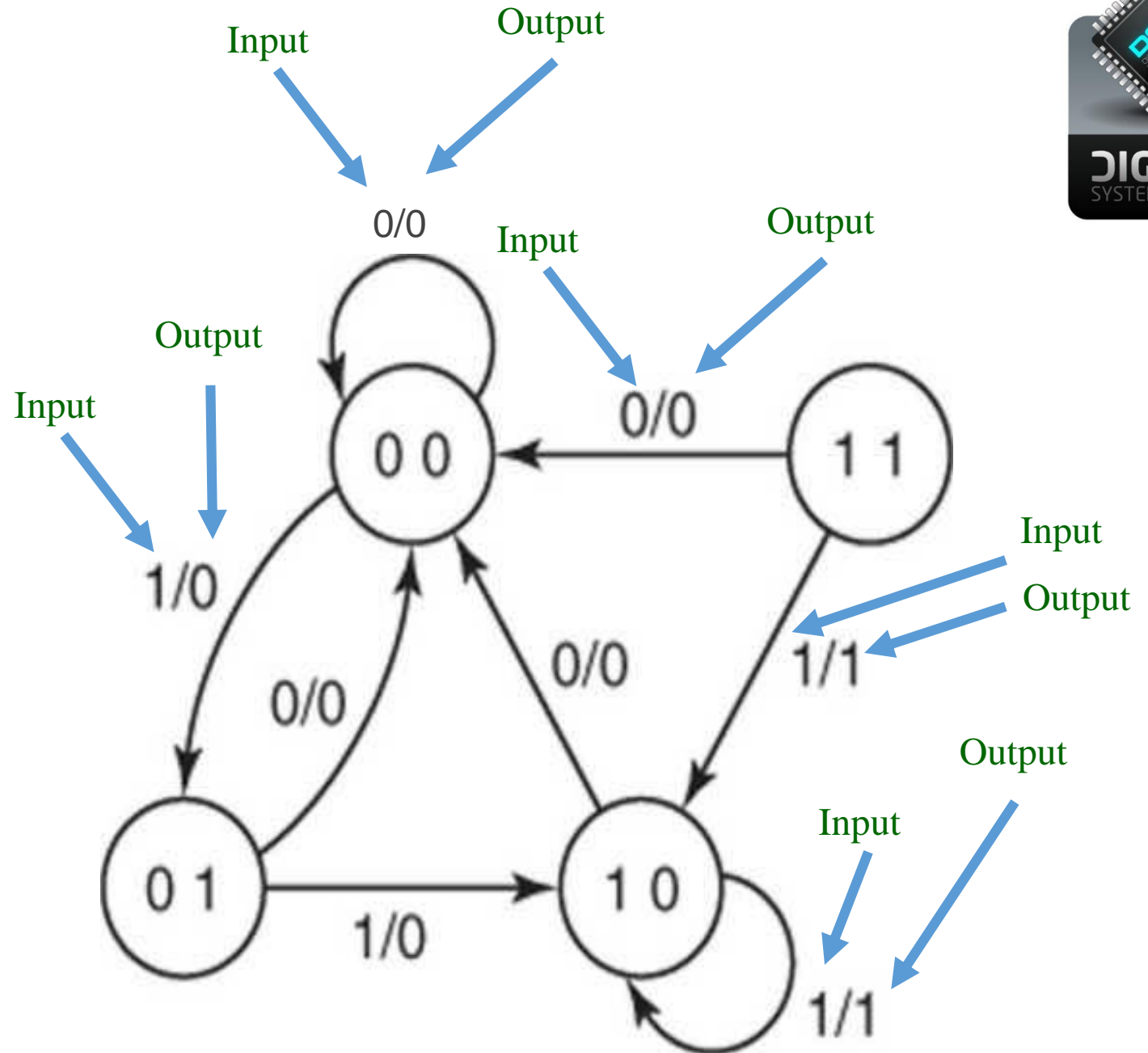

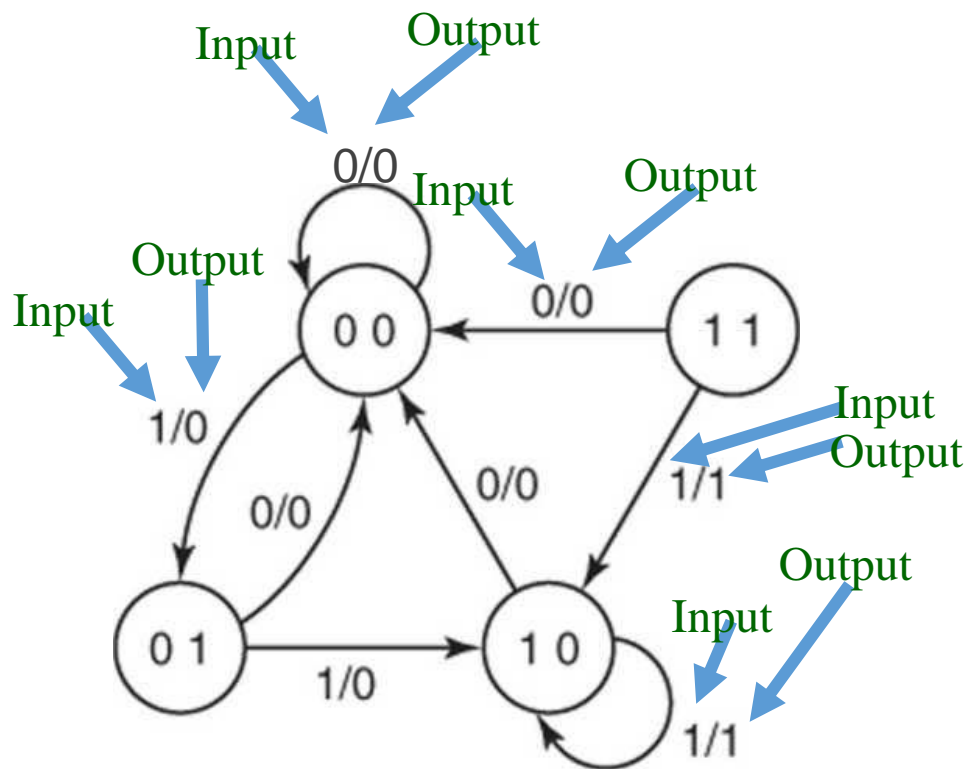Example 1




Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,



The ckt input			Next state		OUTPUT Z
Input	Current state				
X=0	A	B	A	B	X=0
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0

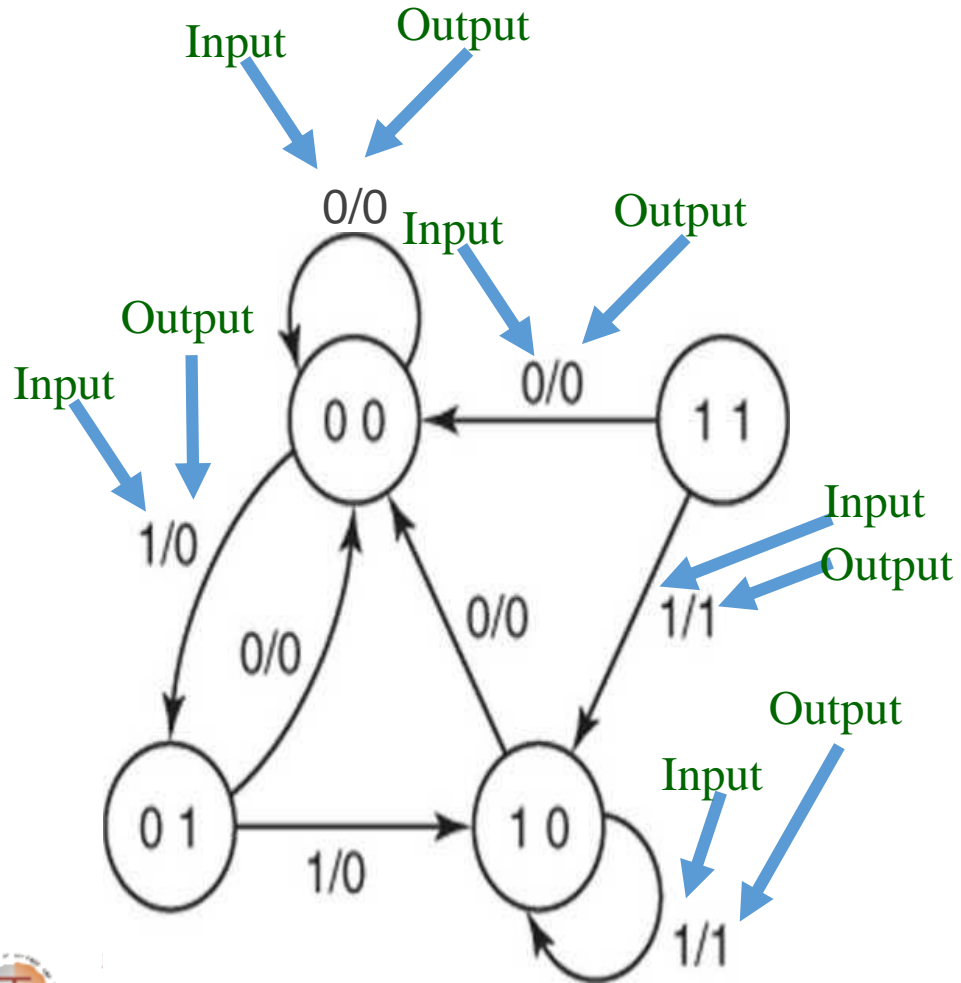Example 1


Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,



The ckt input					
Input	Current state		Next state		OUTPUT Z
X=1	A	B	A	B	X=1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	0	1

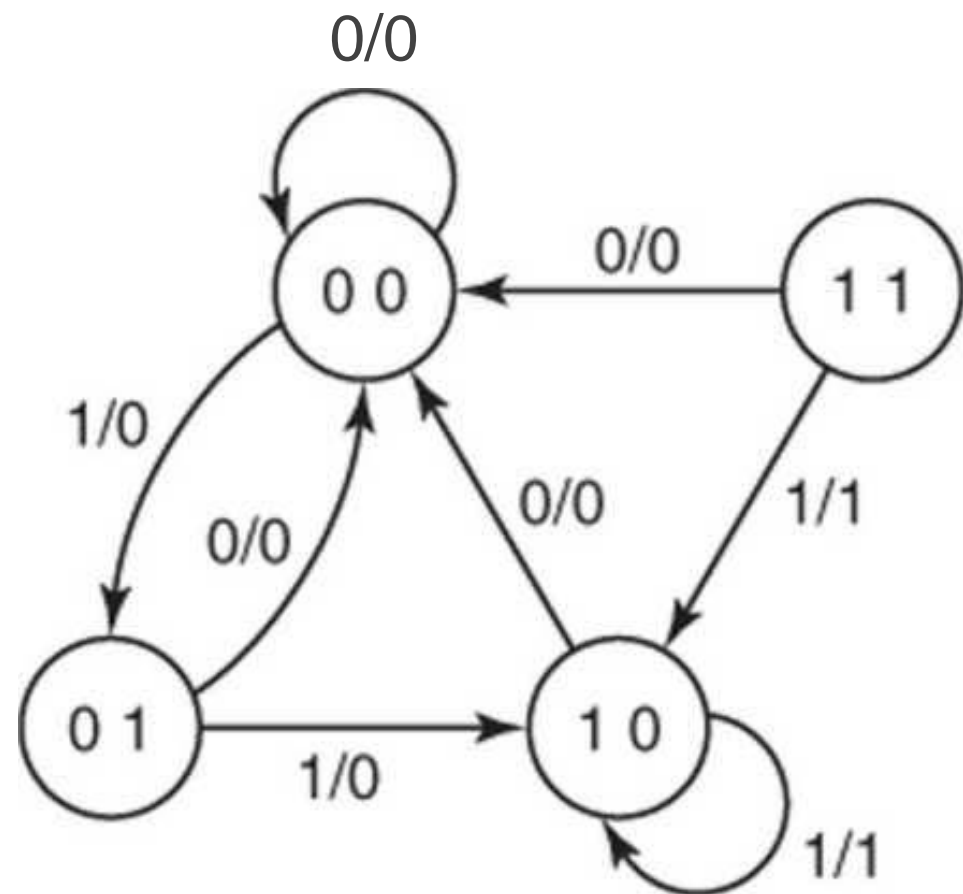Example 1

Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,




The ckt input			Next state		OUTPUT Z
Input	Current state				
X=0	A	B	A	B	X=0
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0

The ckt input			Next state		OUTPUT Z
Input	Current state				
X=1	A	B	A	B	X=1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	0	1

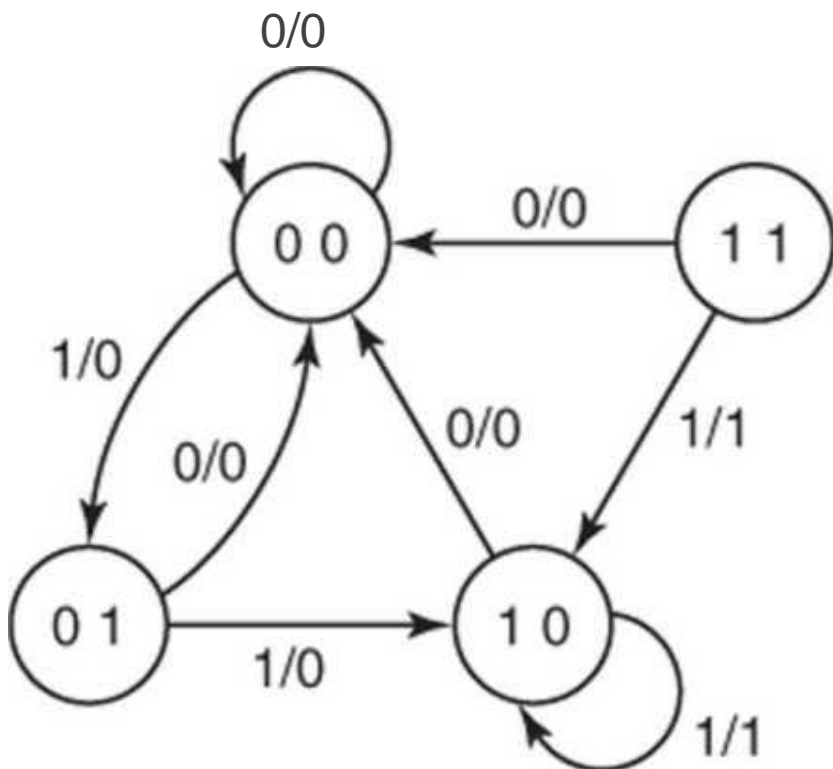Example 1

Design the circuit with the help of D flip Flop and write the State Table for the below State Diagram,



q	q^*		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$A \ B$	$A \ B$	$A \ B$		
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	0 0	1 0	0	1
1 1	0 0	1 0	0	1

D-FF characteristic eq: $D = Q^*$

Example 1

		AB			
		00	01	11	10
D_A	x				
		00	01	11	10
0	0	0	0	0	0
1	1	0	1	1	1

$$D_A = Ax + Bx$$

A	B	X
0	1	1
1	0	1
1	1	1

		AB			
		00	01	11	10
D_B	x				
		00	01	11	10
0	0	0	0	0	0
1	1	1	0	0	0

$$D_B = A'B'x$$

A	B	X
0	0	1

		AB			
		00	01	11	10
Z	x				
		00	01	11	10
0	0	0	0	0	0
1	1	0	0	1	1

$$z = Ax$$

A	B	X
1	1	1
1	0	1




		q^*		z	
		$x=0$	$x=1$	$x=0$	$x=1$
A	B	A	B	A	B
		A	B	A	B
0	0	0	0	0	0
0	1	0	0	0	0
1	0	0	0	0	1
1	1	0	0	0	1

D-FF characteristic eq: $D = Q^*$


Example 1

Design circuit

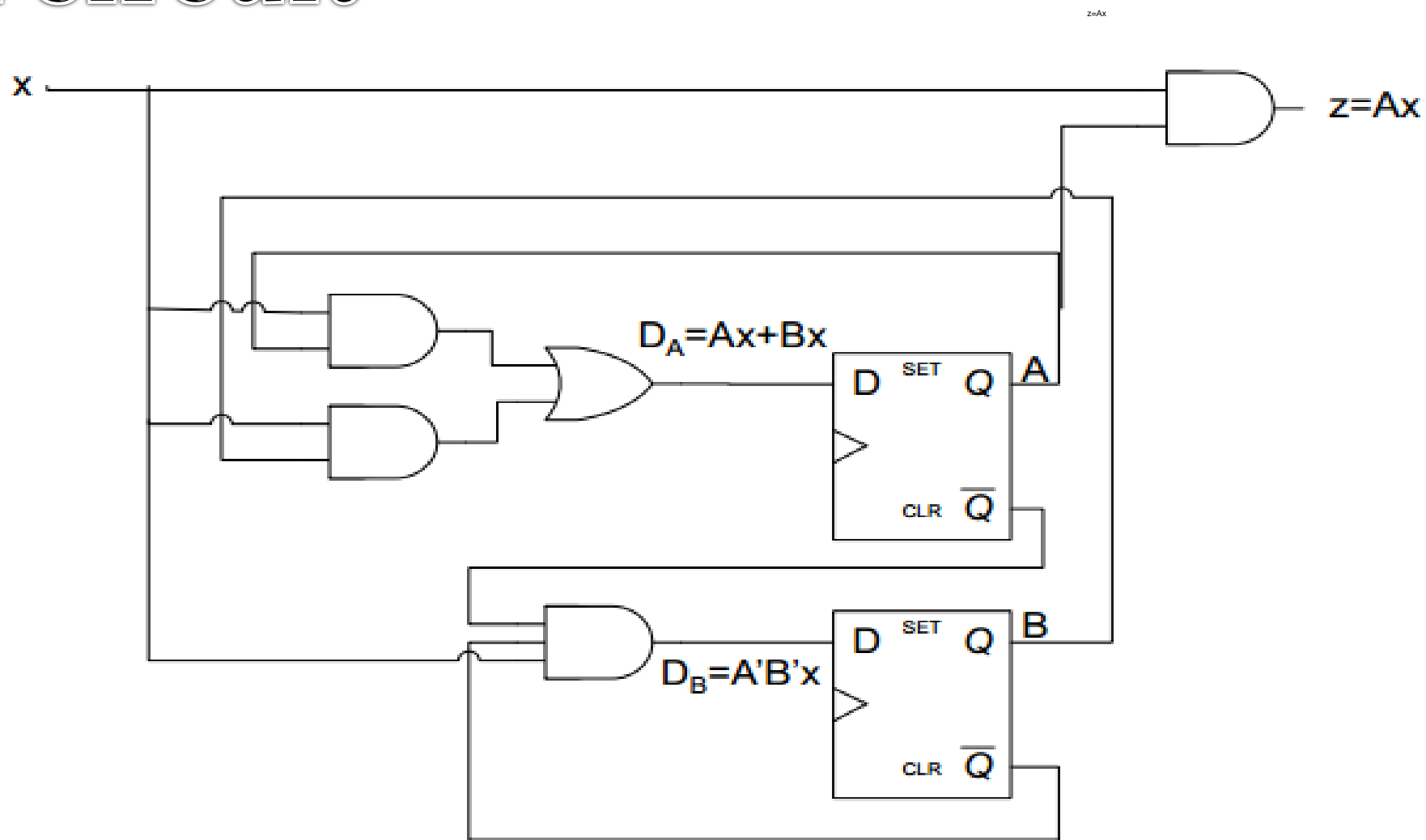

Example 2

Show the state diagram of following circuit

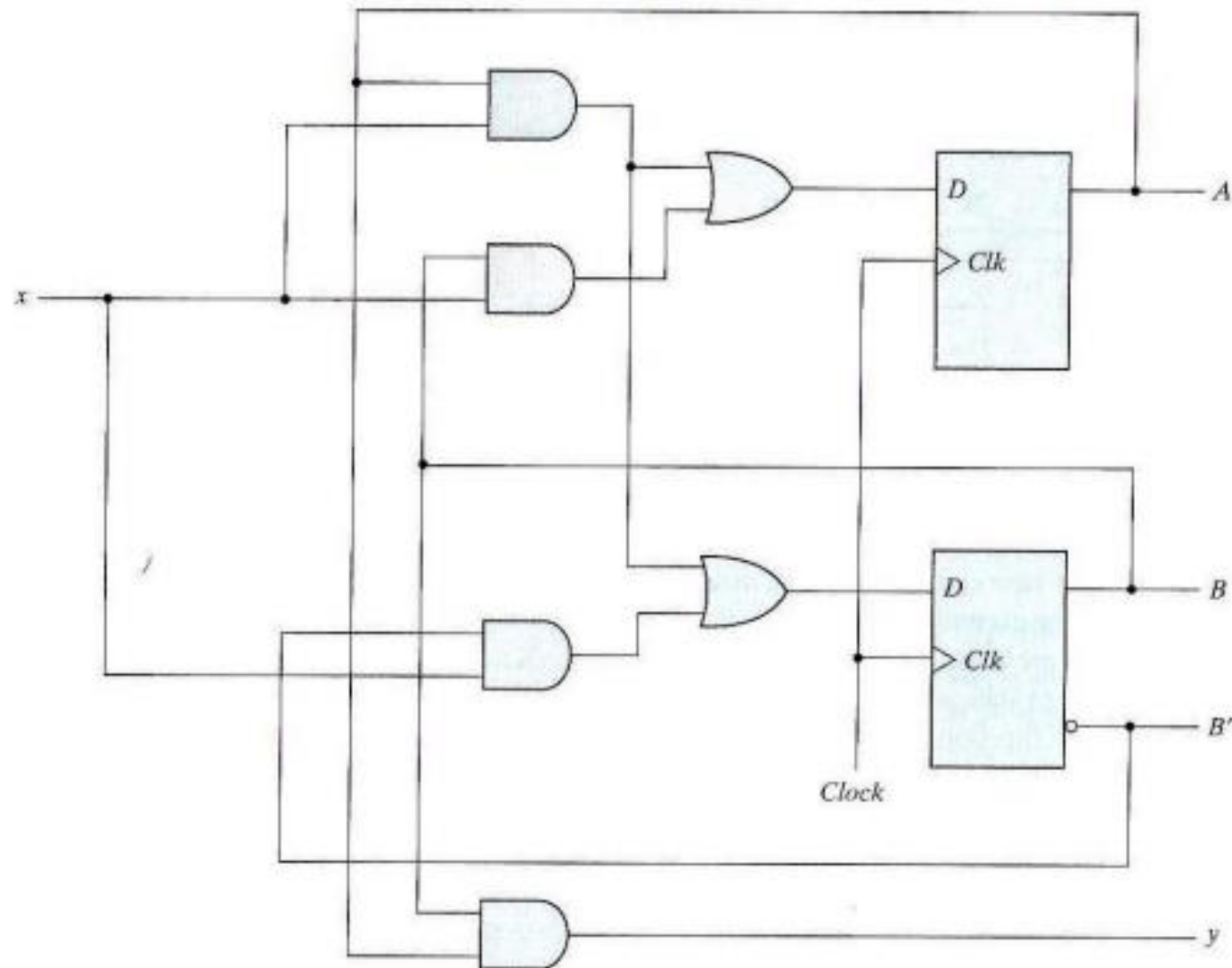

Example 2

Show the state diagram of following circuit


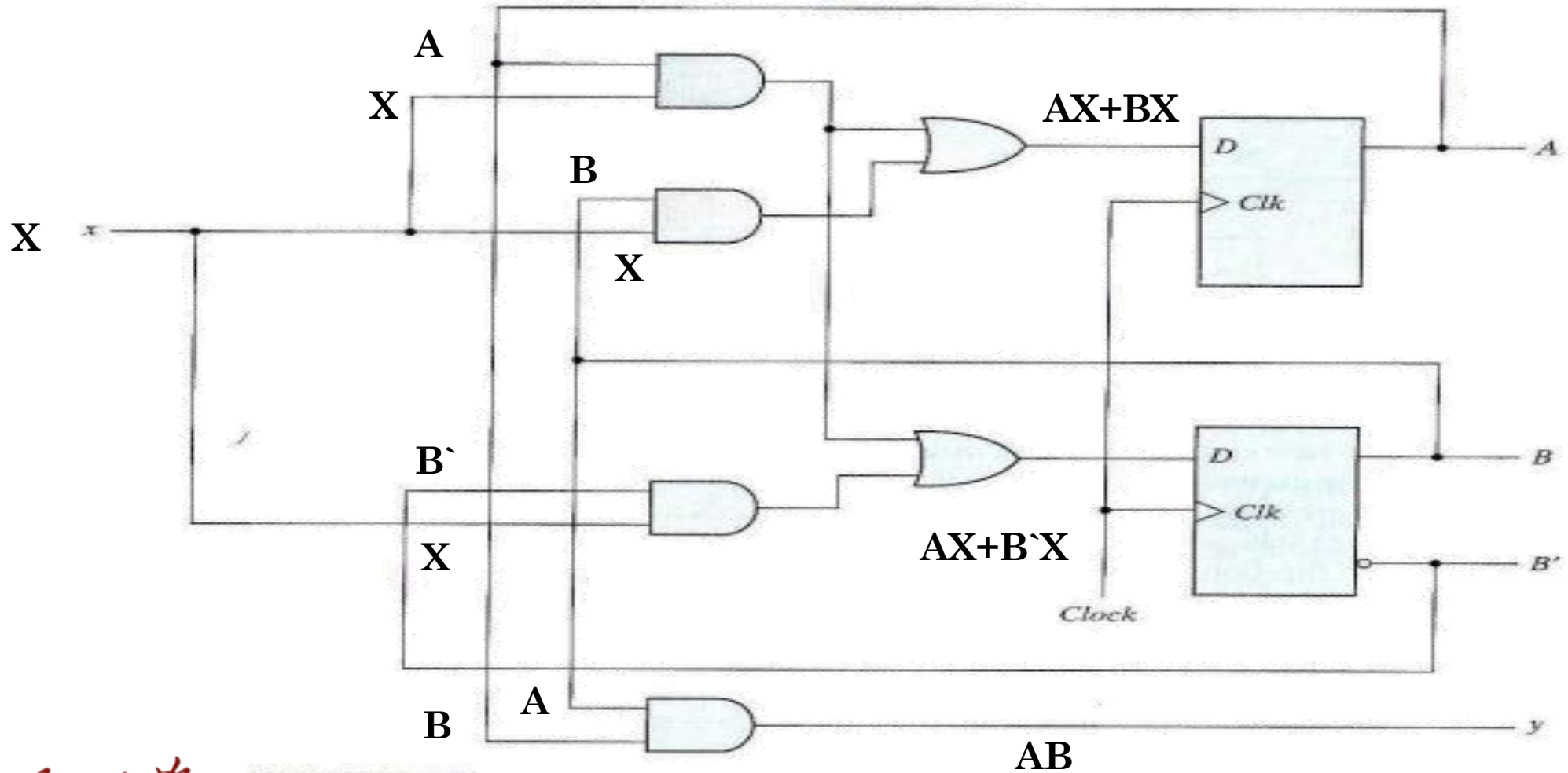


FIGURE 5.29
Logic diagram of sequence detector

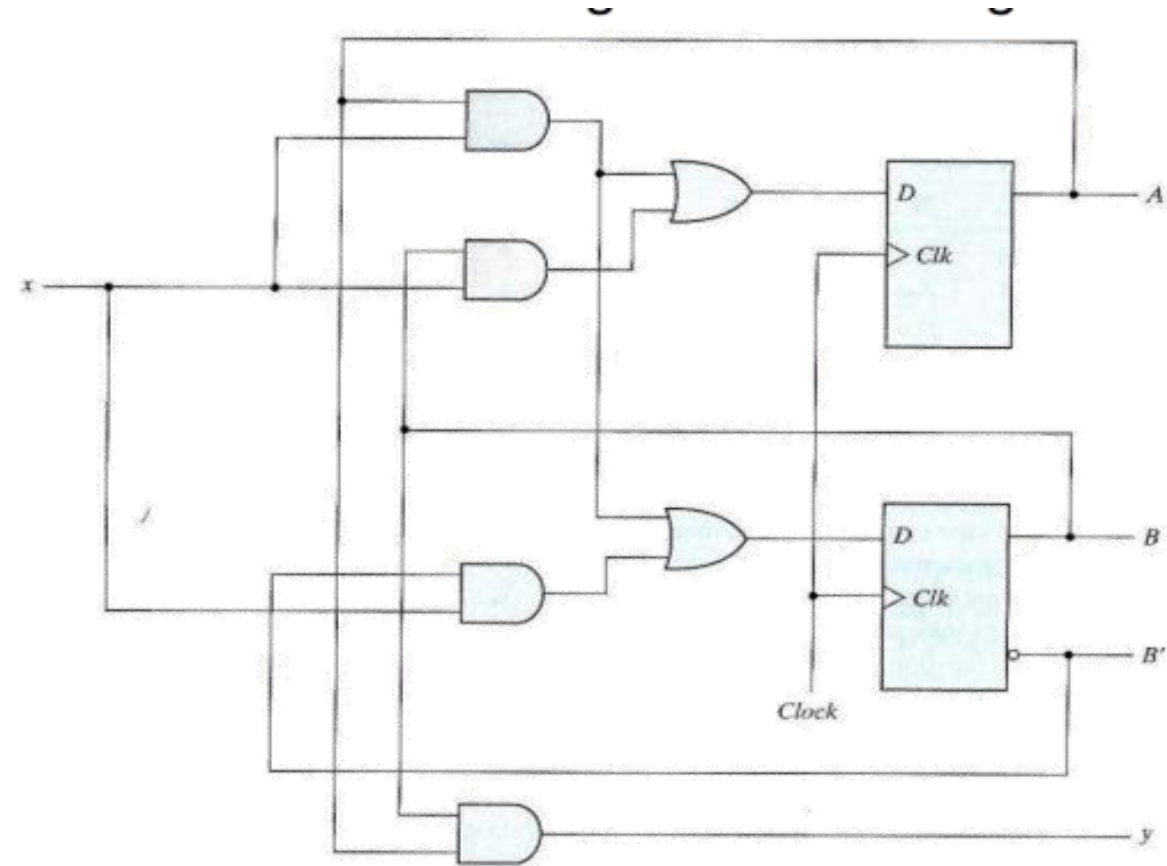Example 2

Show the state diagram of following circuit



$$y = AB$$
$$D_A = Ax+Bx$$
$$D_B = Ax+B'x$$

$$y = AB$$
$$D_A = Ax+Bx$$
$$D_B = Ax+B'x$$

x: input, y: output
A, B: present state
 D_A, D_B : next state (D-FF)


FIGURE 5.29
Logic diagram of sequence detector

Example 2

The ckt input			Next state		OUTPUT Y
Input	Current state				
X=0	A	B	A	B	X=0
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	1


The ckt input			Next state		OUTPUT Y
Input	Current state				
X=1	A	B	A	B	X=1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	1	1	1

Example 2

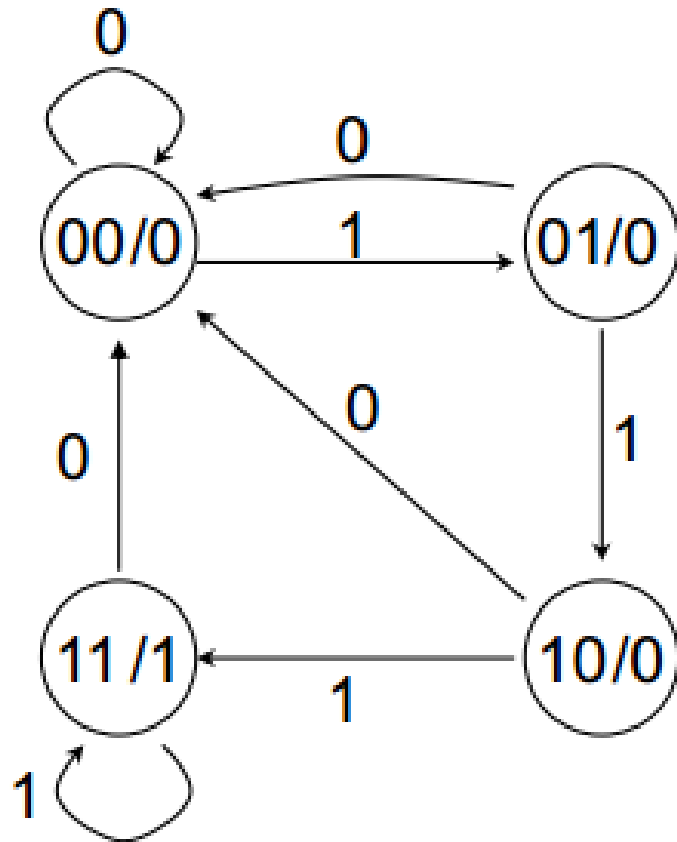

Present State		Next State				Output
		$x = 0$		$x = 1$		
A	B	A	B	A	B	Y
0	0	0	0	0	1	0
0	1	0	0	1	0	0
1	0	0	0	1	1	0
1	1	0	0	1	1	0
		0	0	1	1	1

Example 2

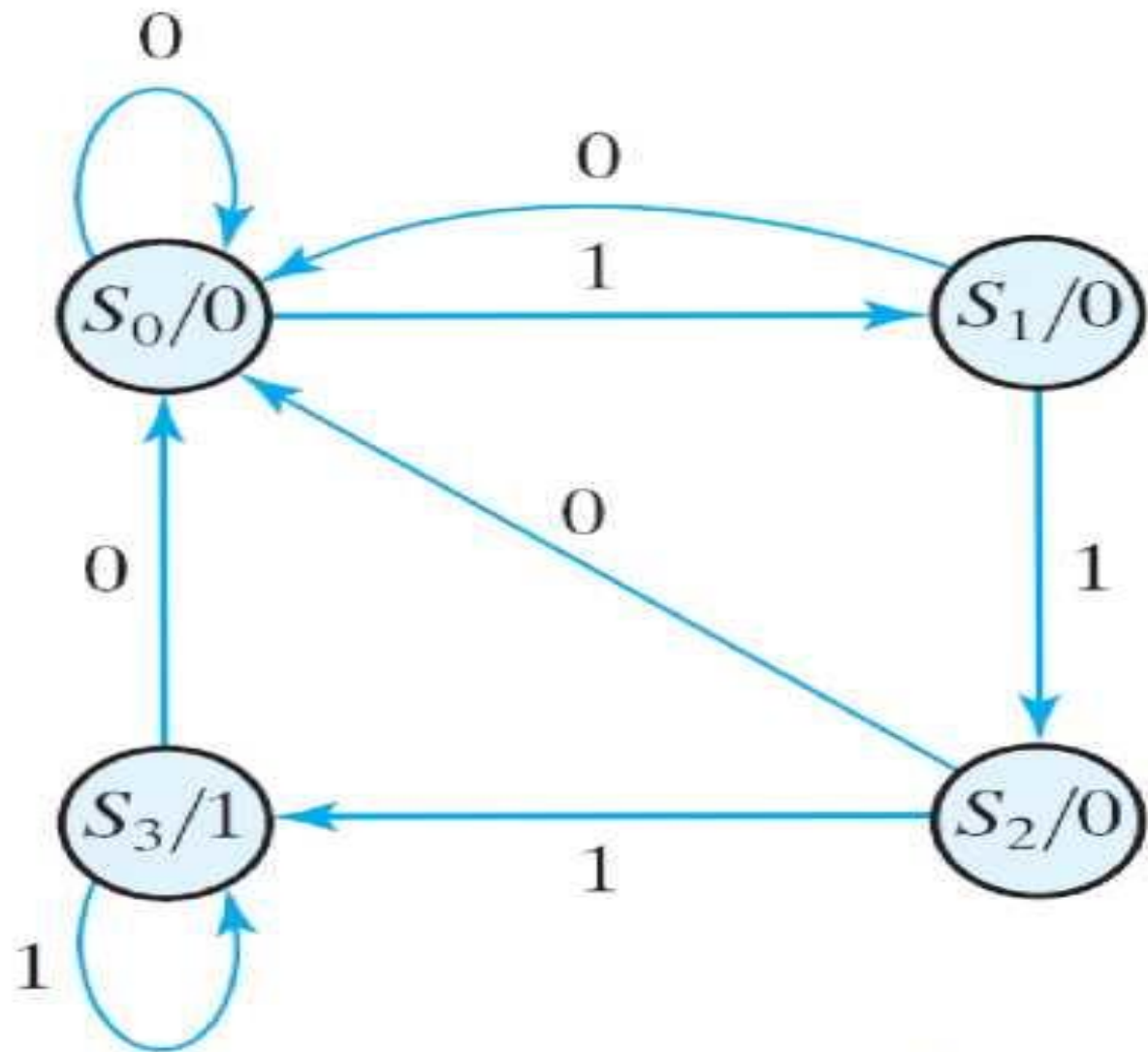

Example 3



Design a 2-bit complex counter with one input x that can be

- a down counter when $x=0$ (... $\rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \rightarrow 11 \rightarrow \dots$)
- a Johnson counter when $x=1$ (... $\rightarrow 00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \rightarrow \dots$)

PRESENT STATE		NEXT STATE	
		x=0	x=1
A	B	A B	A B
0	0	1 1	0 1
0	1	0 0	1 1
1	0	0 1	0 0
1	1	1 0	1 0

Example 3

PRESENT STATE		NEXT STATE	
		x=0	x=1
A	B	A B	A B
0	0	1 1	0 1
0	1	0 0	1 1
1	0	0 1	0 0
1	1	1 0	1 0

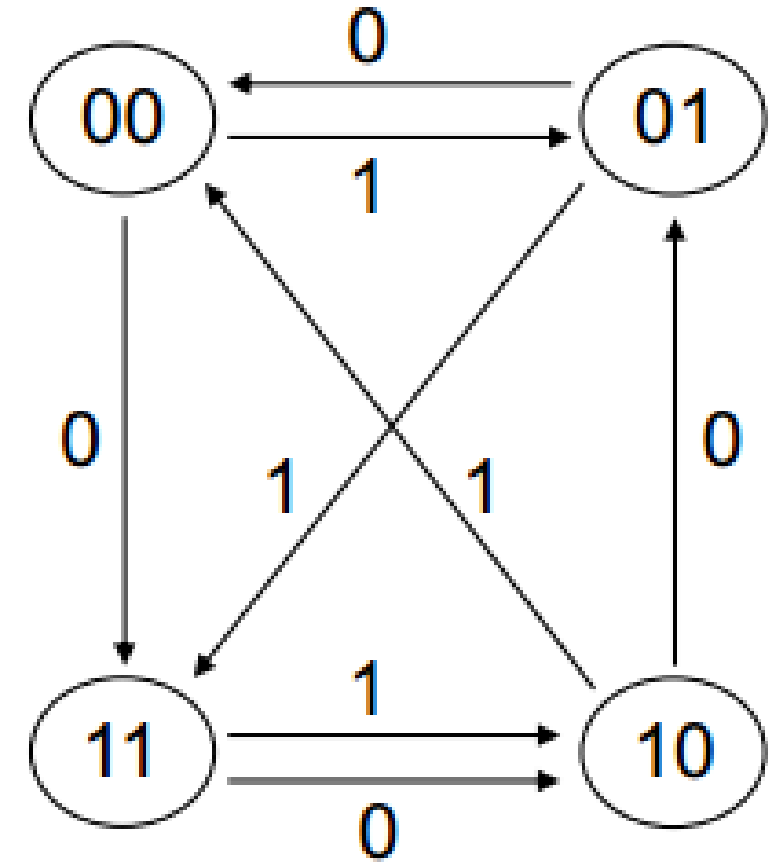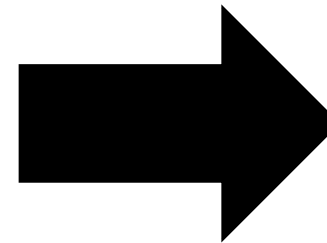

Example 3

PRESENT STATE		NEXT STATE			
		x=0		x=1	
A	B	A	B	A	B
0	0	1	1	0	1
0	1	0	0	1	1
1	0	0	1	0	0
1	1	1	0	1	0

D_A

x \ AB				
	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$$D_A = AB + Bx + A'B'x'$$

Example 3


PRESENT STATE		NEXT STATE			
		x=0		x=1	
A	B	A	B	A	B
0	0	1	1	0	1
0	1	0	0	1	1
1	0	0	1	0	0
1	1	1	0	1	0

D_B

x \ AB				
	00	01	11	10
0	1	0	0	1
1	1	1	0	0

$$D_B = B'x' + A'x$$

Example 3

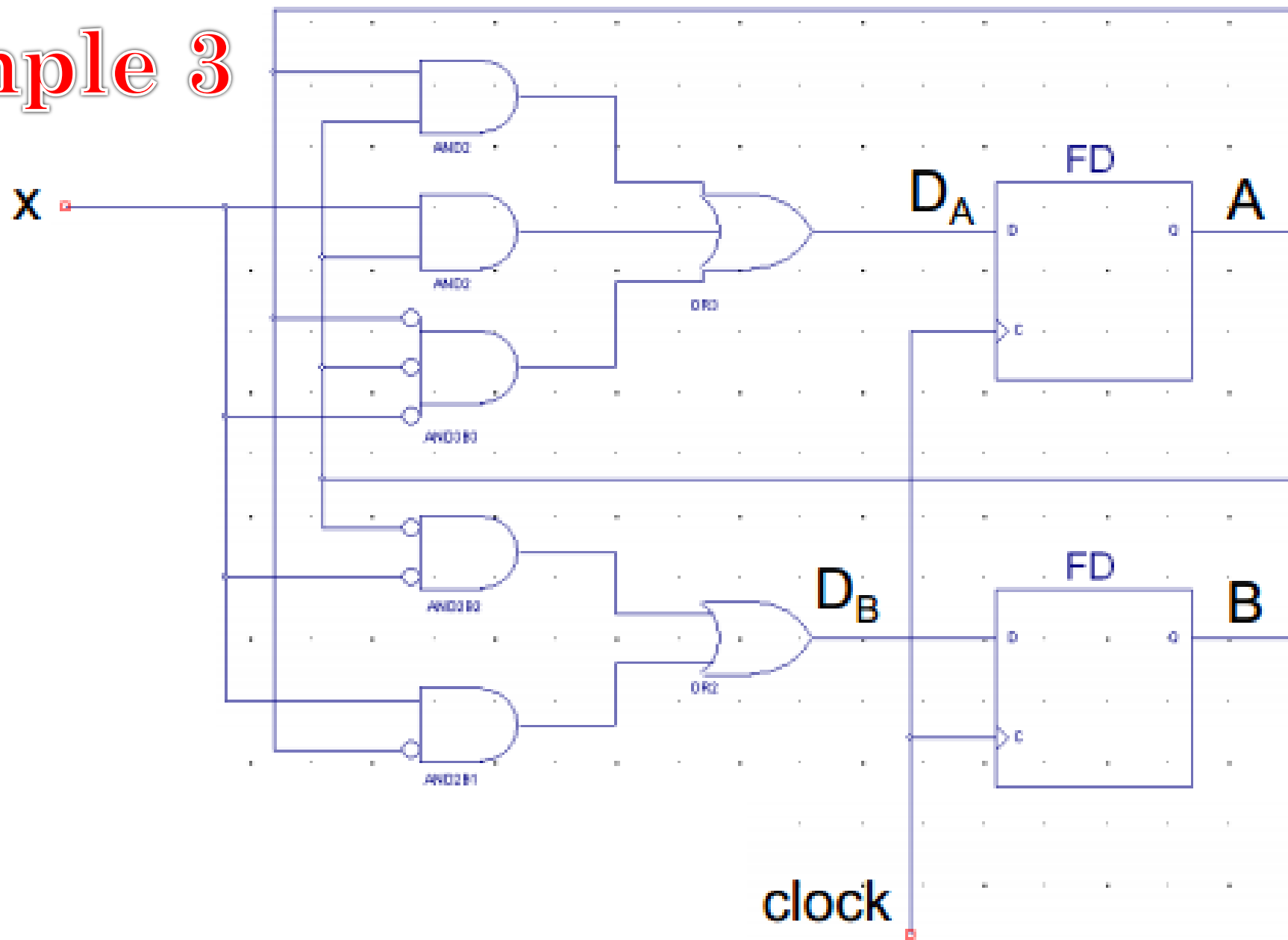

Reference

