

江西理工大学

Jiangxi University of Science and Technology

信息工程学院

School of information engineering





Spring_2020





Prof Associate, School of information engineering Jiangxi university of science and technology, China

EMAIL: ajm@jxust.edu.cn



Jiangxi University of Science and Technology

Sequential circuits Registers /Shift registers



What is register & what is shift registers





- Flip-flop is a 1 bit memory cell which can be used for storing the digital data. To increase the storage capacity in terms of number of bits, we have to use a group of flip-flop. Such a group of flip-flop is known as a **Register**. The **n-bit register** will consist of **n** number of flip-flop and it is capable of storing an **n-bit** word.
- The binary data in a register can be moved within the register from one flip-flop to another. The registers that allow such data transfers are called as **shift registers**. There are four mode of operations of a shift register.
- Serial Input Serial Output
- Serial Input Parallel Output
- Parallel Input Serial Output
- Parallel Input Parallel Output



Basic Register

 - Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- Register: multiple flip-flops sharing clock signal
 - From this point, we'll use registers for bit storage
 - No need to think of latches or flip-flops
 - But now you know what's inside a register



 







Serial Input Serial Output



- Let all the flip-flop be initially in the reset condition i.e. $Q_3 = Q_2 = Q_1 = Q_0 = 0$.
- If an entry of a four bit binary number 1 1 1 1 is made into the register, this number should be applied to $\mathbf{D_{in}}$ bit with the LSB bit applied first.
- The D input of FF-3 i.e. D_3 is connected to serial data input D_{in} . Output of FF-3 i.e. Q_3 is connected to the input of the next flip-flop i.e. D_2 and so on.

 


 

Operation



 
- Before application of clock signal, let $Q_3 Q_2 Q_1 Q_0 = 0000$ and apply LSB bit of the number to be entered to D_{in} . So $D_{in} = D_3 = 1$.
- Apply the clock. On the first falling edge of clock, the FF-3 is set, and stored word in the register is Q_3Q_2 Q_1 $Q_0 = 1000$.







 
- Apply the next bit to D_{in} . So $D_{in} = 1$.
- As soon as the next negative edge of the clock hits, FF-2 will set and the stored word change to $Q_3 Q_2 Q_1 Q_0 = 1100$.







 
• Apply the next bit to be stored i.e. 1 to D_{in} . Apply the clock pulse. As soon as the third negative clock edge hits, FF-1 will be set and output will be modified to Q_3 Q_2 Q_1 $Q_0 = 1110$.







 
• Similarly with $D_{in} = 1$ and with the fourth negative clock edge arriving, the stored word in the register is $Q_3 Q_2 Q_1 Q_0 = 1111$.






Truth Table/Waveforms



 

 




Serial Input Parallel Output

DIGITAL SYSTEMS DESIGN

- In such types of operations, the data is entered serially and taken out in parallel fashion. Data is loaded bit by bit.
- The outputs are disabled as long as the data is loading.
- As soon as the data loading gets completed, all the flip-flops contain their required data, the outputs are enabled so that all the loaded data is made available over all the output lines at the same time.
- 4 clock cycles are required to load a four bit word. Hence the speed of operation of SIPO mode is same as that of SISO mode.

 



Parallel Input Serial Output (PISO)



12

- Data bits are entered in parallel fashion.
- The circuit shown below is a four bit parallel input serial output register.
- Output of previous Flip Flop is connected to the input of the next one via a combinational circuit.
- The binary input word B_0 , B_1 , B_2 , B_3 is applied though the same combinational circuit.
- There are two modes in which this circuit can work namely shift mode or load mode.

Load mode

When the shift/load bar line is low (0), the AND gate 2, 4 and 6 become active they will pass B_1 , B_2 , B_3 bits to the corresponding flip-flops. On the low going edge of clock, the binary input B_0 , B_1 , B_2 , B_3 will get loaded into the corresponding flip-flops. Thus parallel loading takes place

Shift mode


When the shift/load bar line is low (1), the AND gate 2, 4 and 6 become inactive. Hence the parallel loading of the data becomes impossible. But the AND gate 1,3 and 5 become active. Therefore the shifting of data from left to right bit by bit on application of clock pulses. Thus the parallel in serial out operation takes place.



DR AJM

Block Diagram



 




Parallel Input Parallel Output (PIPO)



 • In this mode, the 4 bit binary input B_0 , B_1 , B_2 , B_3 is applied to the data inputs D_0 , D_1 , D_2 , D_3 respectively of the four flip-flops. As soon as a negative clock edge is applied, the input binary bits will be loaded into the flip-flops simultaneously. The loaded bits will appear simultaneously to the output side. Only clock pulse is essential to load all the bits.






Bidirectional Shift Register



- If a binary number is shifted left by one position then it is equivalent to multiplying the original number by 2. Similarly if a binary number is shifted right by one position then it is equivalent to dividing the original number by 2.
- Hence if we want to use the shift register to multiply and divide the given binary number, then we should be able to move the data in either left or right direction.
- Such a register is called bi-directional register. A four bit bi-directional shift register is shown in fig.
- There are two serial inputs namely the serial right shift data input DR, and the serial left shift data input DL along with a mode select input (M).



Mode control (M)

 





Operation



S.N	Condition	Operation
1	With M = 1 - Shift right operation	If $M=1$, then the AND gates 1, 3, 5 and 7 are enabled whereas the remaining AND gates 2, 4, 6 and 8 will be disabled. The data at D_R is shifted to right bit by bit from FF-3 to FF-0 on the application of clock pulses. Thus with $M=1$ we get the serial right shift operation.
2	With M = 0 - Shift left operation	When the mode control M is connected to 0 then the AND gates 2, 4, 6 and 8 are enabled while 1, 3, 5 and 7 are disabled. The data at D_L is shifted left bit by bit from FF-0 to FF-3 on the application of clock pulses. Thus with $M=0$ we get the serial right shift operation.



Universal Shift Register




- A shift register which can shift the data in only one direction is called a uni-directional shift register. A shift register which can shift the data in both directions is called a bi-directional shift register. Applying the same logic, a shift register which can shift the data in both directions as well as load it parallely, is known as a universal shift register. The shift register is capable of performing the following operation
 - Parallel loading
 - Left Shifting
 - Right shifting
- The mode control input is connected to logic 1 for parallel loading operation whereas it is connected to 0 for serial shifting. With mode control pin connected to ground, the universal shift register acts as a bi-directional register. For serial left operation, the input is applied to the serial input which goes to AND gate-1 shown in figure. Whereas for the shift right operation, the serial input is applied to D input.



DR AJM




 



The block Diagram of shift registor




 



 The simple Shift register with D flip flop








Basic shift register



 A basic shift register is simply a chain of *D* flip-flops with a common clock.



Each flip-flop transfers its *D* input to its *Q* output at a clock transition.


- The effect is to transfer data along the register, one flip-flop per clock cycle.
- This type of register is called a serial input-serial output (SISO).



Basic shift register

 A basic shift register is simply a chain of D flip-flops with a common clock.





The table shows the contents of the register after successive clock transitions. The assumption is that the register is initially clear.

- The number of clock pulses needed to fill the register is equal to the number of flip-flops used to make the register.
 - This is a 4 bit register.


serial	
output	_

	input	Q_{A}	Q_{B}	$Q_{\rm C}$	Q_{D}
ī	0	0	0	0	0
	1	1	0	0	0
es	1	1	1	0	0
slne	1	1	1	1	0
clock pulses	0	0	1	1	1
-clo	0	0	0	1	1
	1	1	0	0	1
\	0	0	1	0	0



Timing for a shift register



 


input	Q_{A}	Q_{B}	$Q_{\rm C}$	Q_{D}
0	0	0	0	0
1	1	0	0	0
1	1	1	0	0
1	1	1	1	0
0	0	1	1	1
0	0	0	1	1
1	1	0	0	1

The pattern in successive flip-flops moves to the right with each clock cycle to shift the pattern into and out of the register.



Timing for a shift register



 

Applications of a basic shift register



- **1. Delay line** N stages delay the signal by N clock cycles
- 2. Multiplication and division by powers of 2, because this just requires a shift of the binary number (like multiplication or division by 10 in decimal)

Example: decimal $3 \times 4 = 12$ becomes $11 \times 100 = 1100$ in binary The arithmetic logic unit (ALU) of a computer processor uses a shift register for this purpose.

Warning: the 'sense' of a shift — left or right — is usually based on its effect on binary numbers written in the usual way. For example,

 $11 \rightarrow 1100$ is called a **left shift**. This is clearer if both numbers are written with 8-bits as $00000011 \rightarrow 00001100$. Similarly, dividing by 2 such as $00010110 \rightarrow 00001011$ is a **right shift**.


This is the opposite of what we usually draw in a counter circuit, with the least significant bit (LSB) on the left. **Take care!**

There is a 'rotate' operation where the output from the shift register is fed back to the beginning, usually through the 'carry bit'.



 
Design of a shift register with JK flip Flop and load PIN





 
Design of a shift register with JK flip Flop and load PIN





 Design of a shift register with the clear and load PIN








SHIFT REGISTER WITH D FLIP FLOP




 



shift register with JK flip Flop



 



Shift registers



Circuit for simple shift register Basic applications

Ring counters Johnson counters

Pseudo-random binary sequences and encryption

Ready-made shift registers are available as integrated circuits, such as the '165

Conversion of data from serial to parallel and vice versa

Large-scale devices such as 'universal asynchronous receiver transmitters' (UARTs) are based on shift registers

Same functions available in microcontrollers ('shift' and 'rotate' instructions)



Reference

mano BOOK

http://osp.mans.edu.eg/cs212/Seq_circuits_analysis.htm

Logic and Computer Design Fundamentals, Charles Kime & Thomas Kaminski © 2008 Pearson Education, Inc.

(Edited by Dr. Muhamed Mudawar for COE 202 and EE 200 at KFUPM)

• https://circuitdigest.com/tutorial/what-is-shift-register-types-applications

